

AY21/22 Semester 1
Issued: Sep. 7, 2021

Problem 1: SRAM memory cell

[illegible]

- a) If $Q = 1$ and $\bar{Q} = 0$ is currently stored in the SRAM cell, and we would like to read the data so that $BL = 1$ and $\bar{BL} = 0$ when WL is applied with “H”, what should be the requirement (width) of $M1$ and $M3$? Why?
- b) Now that $W1$ and $W3$ are determined from a). If $Q = 1$ and $\bar{Q} = 0$ is currently stored in the SRAM cell, and we would like to write “ $Q = 0, \bar{Q} = 1$ ” into the cell, then what is the requirement (width) of $M2$ and $M4$?

Problem 2: DRAM operation

In a 1T DRAM cell shown in Fig. 2, BL is precharged to $V_{BL} = V_{ccA}/2 = 1\text{ V}$, and C_S is initially discharged to GND. Assume $C_S = 20\text{fF}$, and $C_{BL} = 80\text{fF}$ and $V_{th,M1} = 0.4\text{V}$. There is NO sense amplifier attached to the BL.

 


Figure 2. A 1T DRAM cell

- (a) When WL is applied with $V_{ccA} = 2\text{V}$, the access transistor $M1$ will turn on. At this point, will the final BL voltage (V_{Final}) increase or drop, compared with the precharge voltage? By how much (in mV)?
- (b) We now want to write data “1” into C_S , by applying BL with $V_{ccA} = 2\text{V}$. If we apply WL with V_{ccA} (2V) to initiate the writing operation, is there any potential issue? If so, what is it? How can we avoid such issue?