 


# Week 5-1



## Introduction to Electronic Memories

# Moore's Law





Source: H. S. P. Wong, HotChips 2019  
see <https://www.youtube.com/watch?v=O5UQ5OG0snM>

# The Memory Wall

  

**On-chip memory (cache) that is smaller in capacity than off-chip memory but a lot closer in performance and speed to the processor helps to reduce number of slow off-chip memory accesses**

# AMD Zen x86-64 Microprocessor

 
 


Source: wikichip.org



  
# AMD Zen x86-64 Microprocessor

FPU: Floating-point unit BPU: Branch prediction unit LSU: Load-store unit Schdlr: Instruction scheduler  
 Decode: Instruction decoder MS ROM: Microcode store ROM L1\$, L2\$: Level 1 and 2 cache





**Memory can occupy as much as > 80% of the die area in modern digital processors!**  
**Tackling design issues in memory (especially standby power consumption)**  
**is crucial in advancing processor technology**

# The Memory Hierarchy

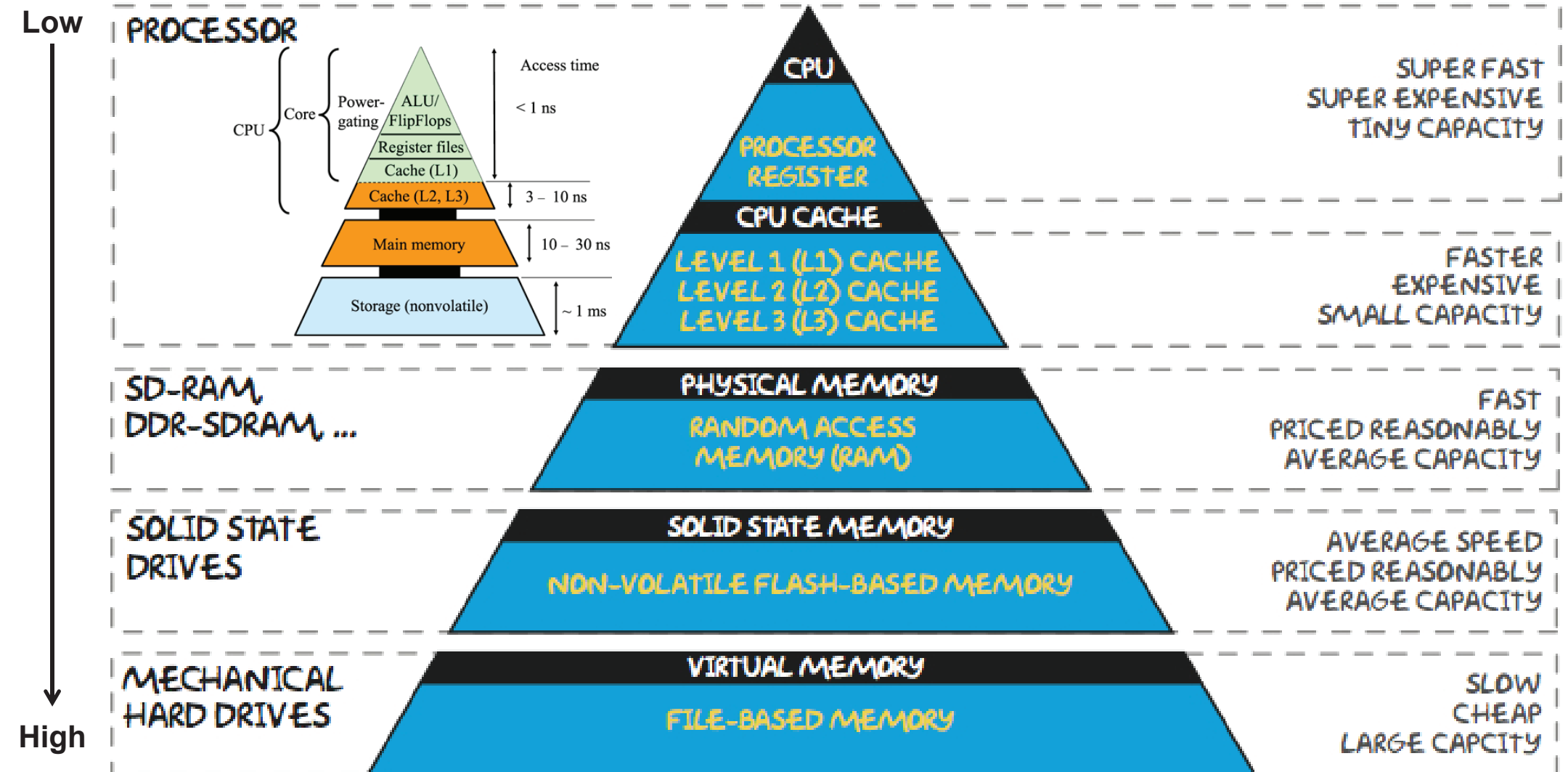


# Logical vs Physical Memory – I

## Logical View of Memory

  

## Physical View of Memory


 


The bitcell array is tall and narrow if it is organized into  $N$  rows by  $M$  columns, with  $N$  and  $M$  corresponding to logical address and width of data word, respectively)


- × Long vertical wires have large parasitics (bad delay)
- × Placement with other circuitry
- × Yield issues in bitcell array and R/W circuitry

# Logical vs Physical Memory – II

## Logical View of Memory

  

## Physical View of Memory

 

The bitcell array is organized into  $N$  rows by  $M$  columns, with  $N$  and  $M$  corresponding to logical address and multiple (usually 8) times the width of data word, respectively


- Bit-interleaved to guard against errors using error-correcting codes (ECC)




# Physical Organization of Memory

## Memory Subsystem

Memory Subsystem I/O Interface

 


## Single Subarray

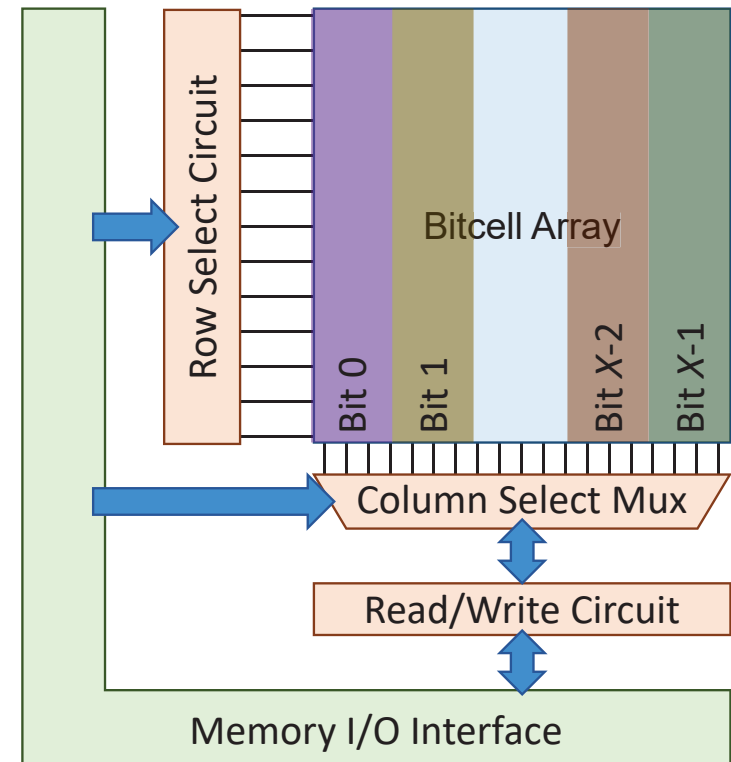

**Memory subsystem is stitched together from many subarrays in a tree like fashion to tradeoff between memory capacity, bandwidth, complexity of control circuitry, power consumption and speed**




# Tradeoffs in Memory Design

 

**Addressing all challenges in memory design requires understanding of interactions across all levels of design abstraction from devices, circuits, architectures, software to applications**

# MOS Memory Classification

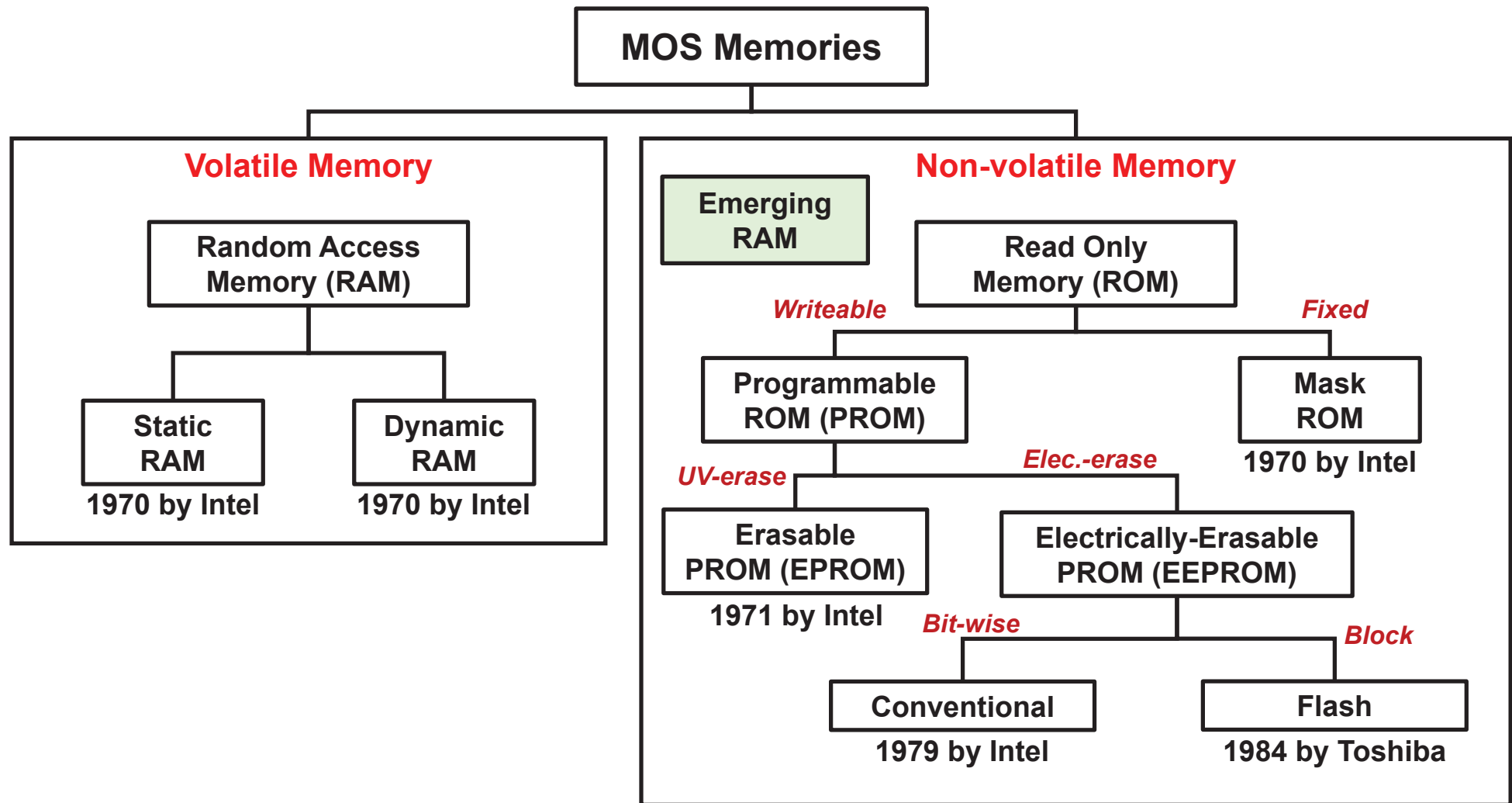


# Week 5-2


Introduction to the 6-Transistor Static RAM (6T SRAM)



# MOS Memory Classification

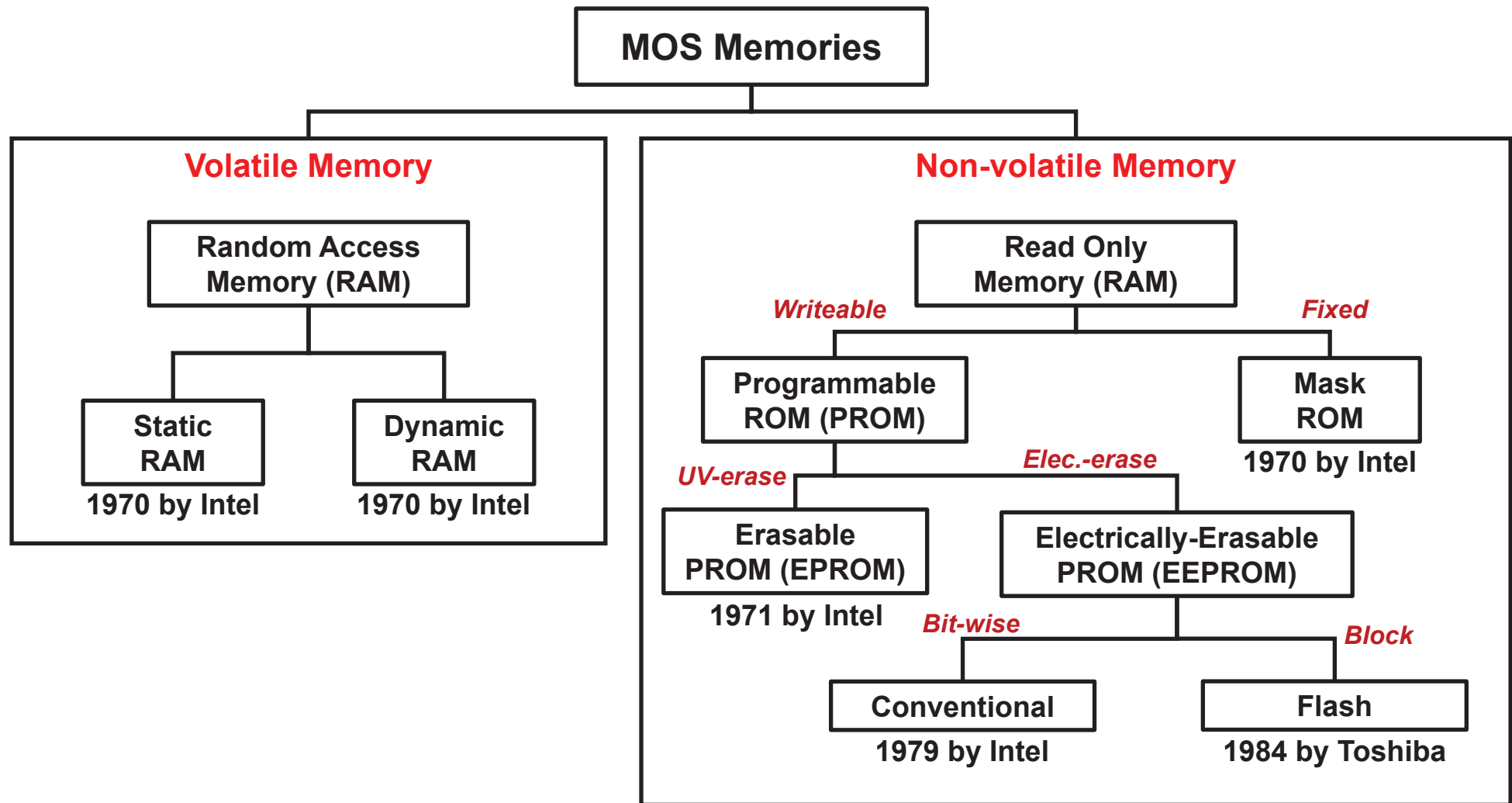

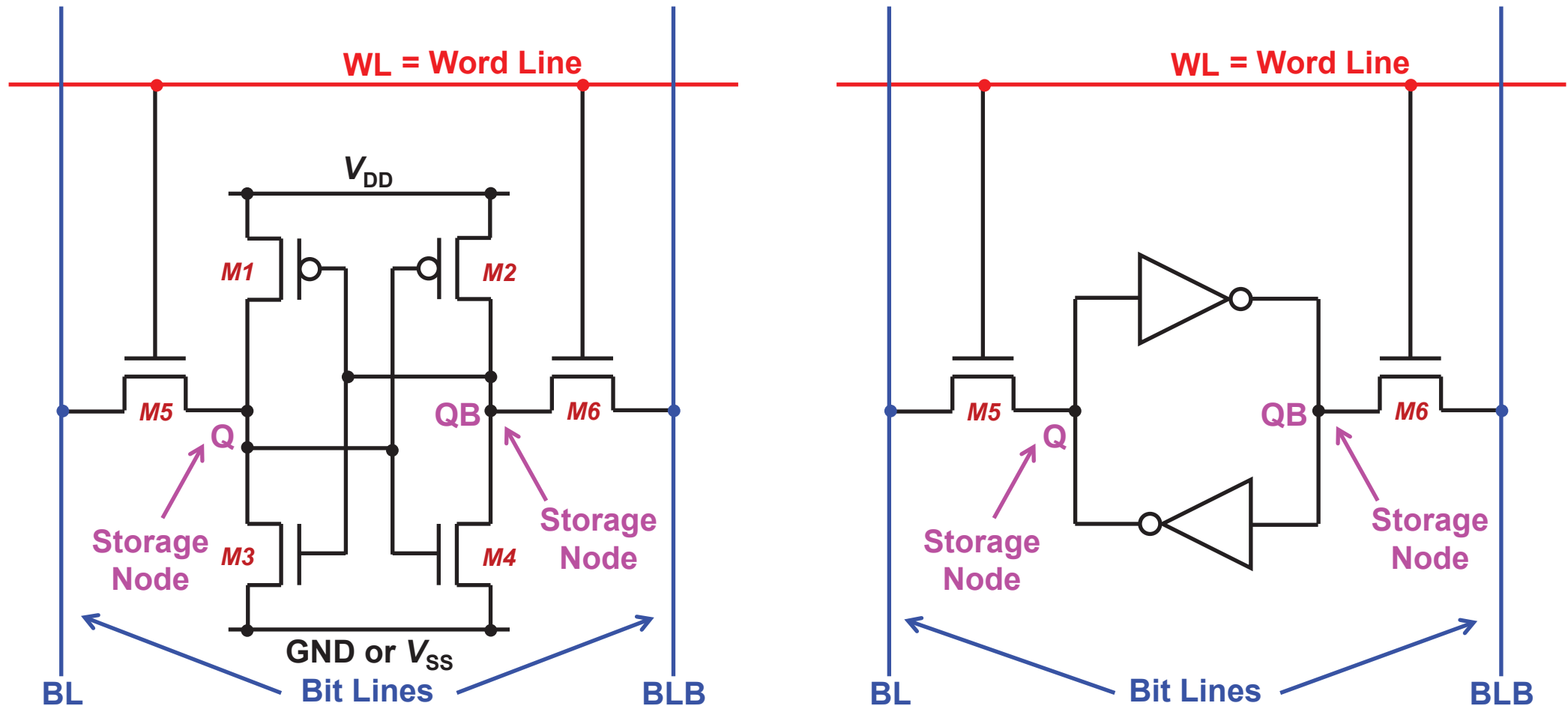
# Bitcell Structure of the 6-Transistor Static RAM (6T SRAM)





Due to symmetry,  $W_{M1}/L_{M1} = W_{M2}/L_{M2}$ ;  $W_{M3}/L_{M3} = W_{M4}/L_{M4}$ ;  $W_{M5}/L_{M5} = W_{M6}/L_{M6}$
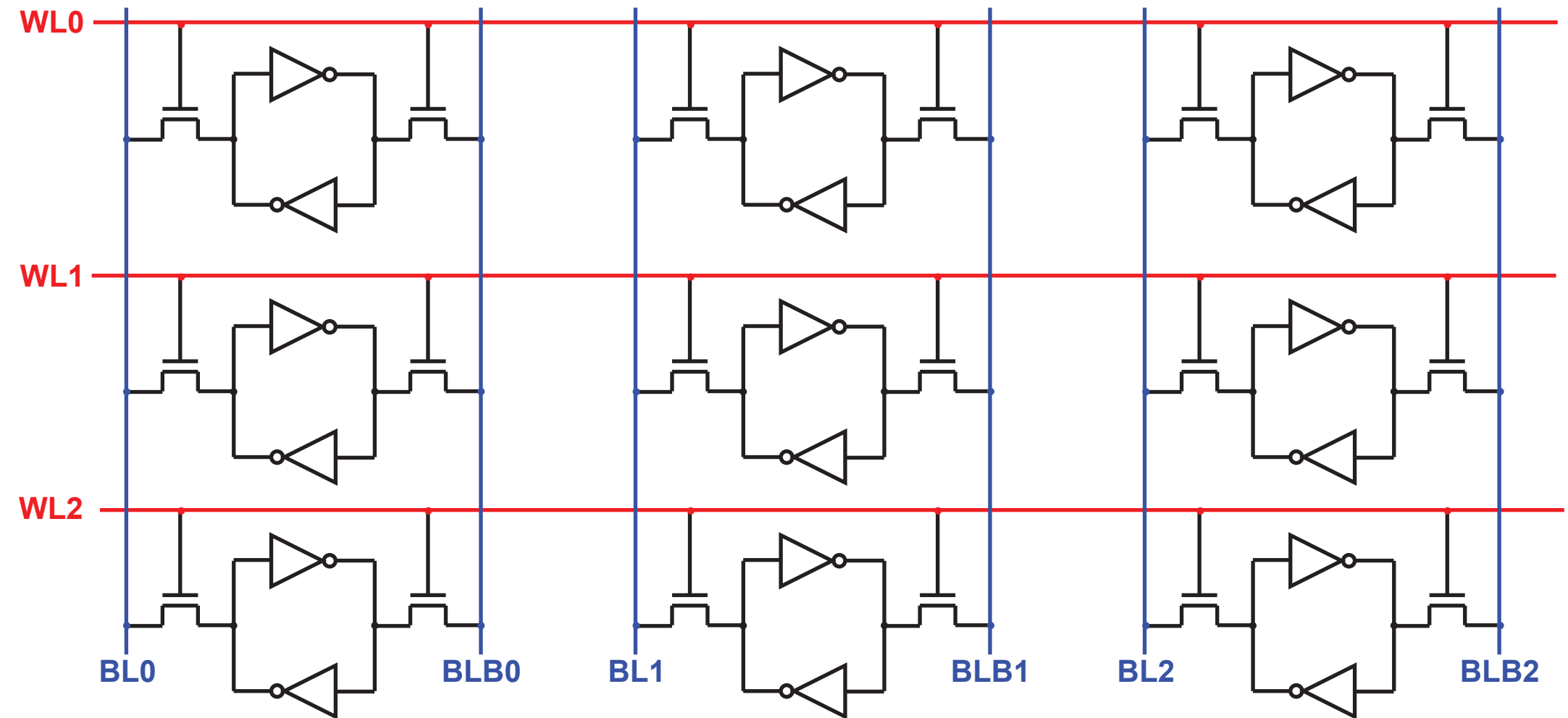
# Array of 6T SRAM Bitcells (Bitcell Array)


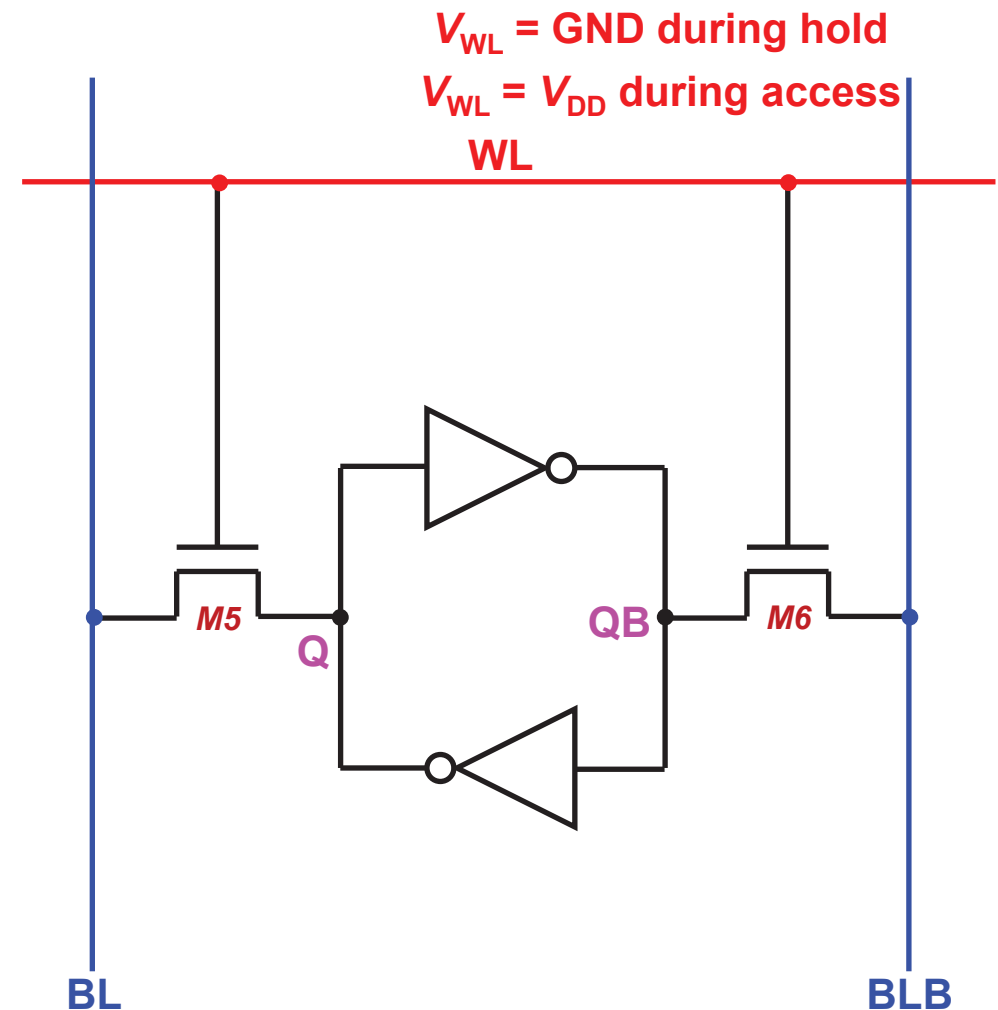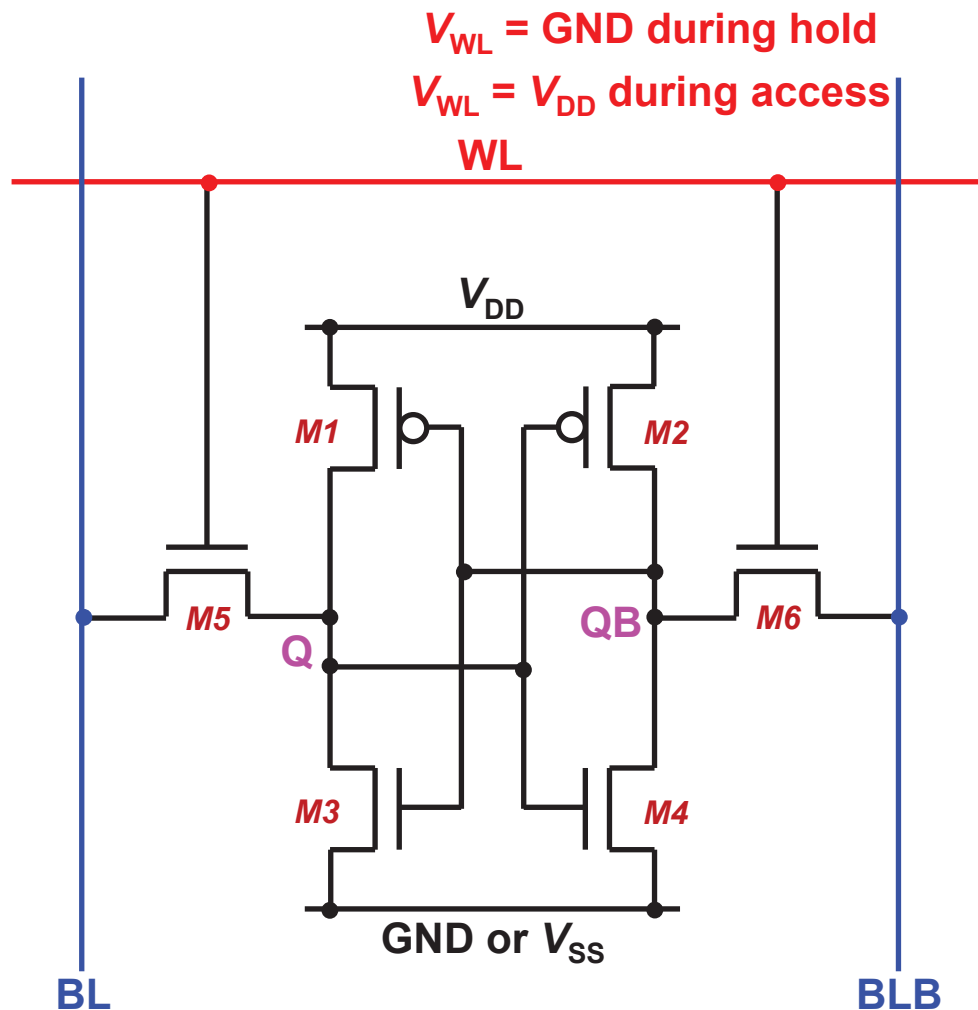
# Bitcell Structure of the 6-Transistor Static RAM (6T SRAM)




- The bitcell is accessed to read from or write into the bitcell
- Otherwise, bitcell is in hold or hold mode and retains its stored data

# Week 5-3



## SRAM Read and Write Operations





# Bitcell Structure of the 6T SRAM

 



# The Bistability Principle

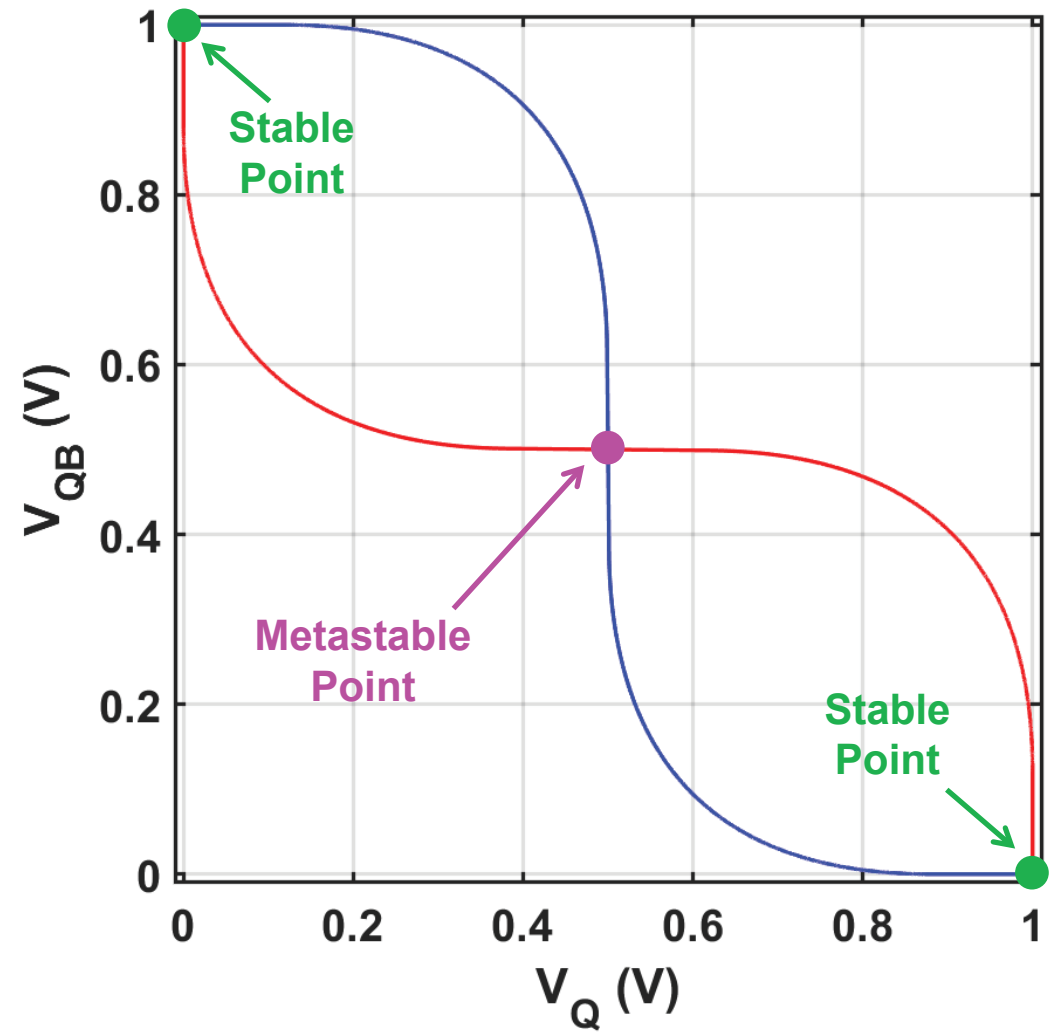 


# The Bistability Principle

  

# The Bistability Principle

  


# Writing Data into the 6T SRAM

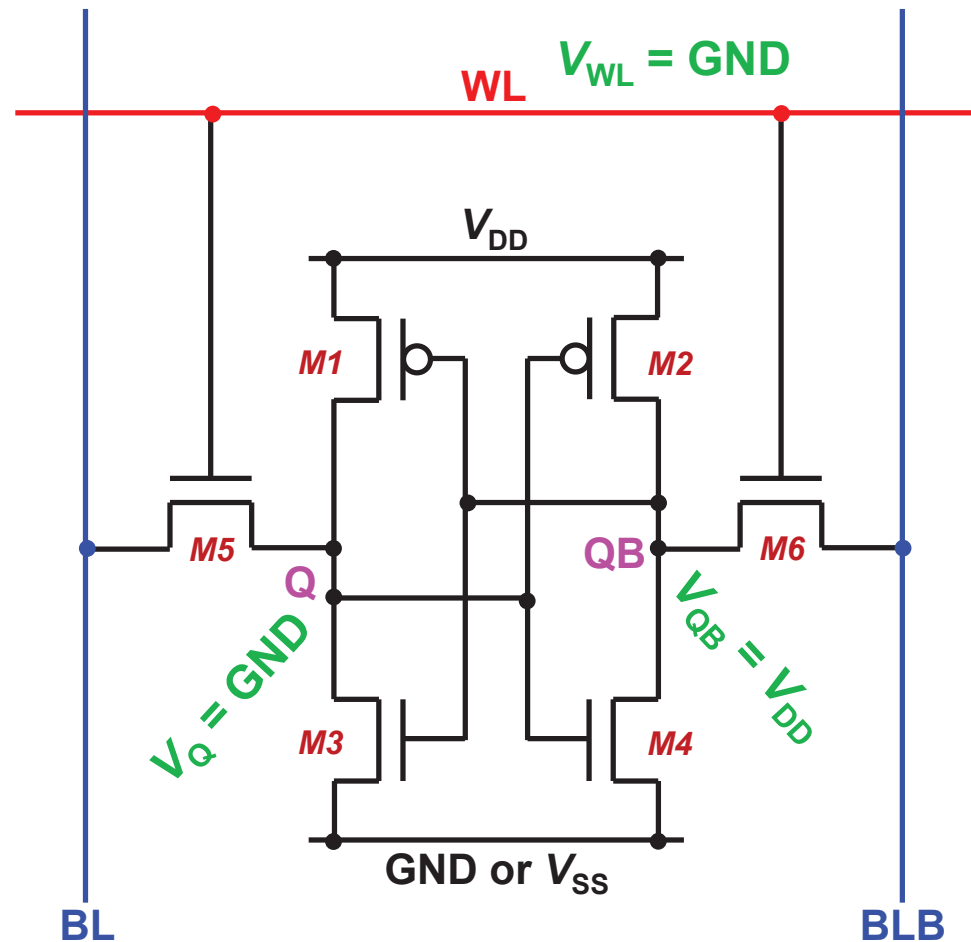




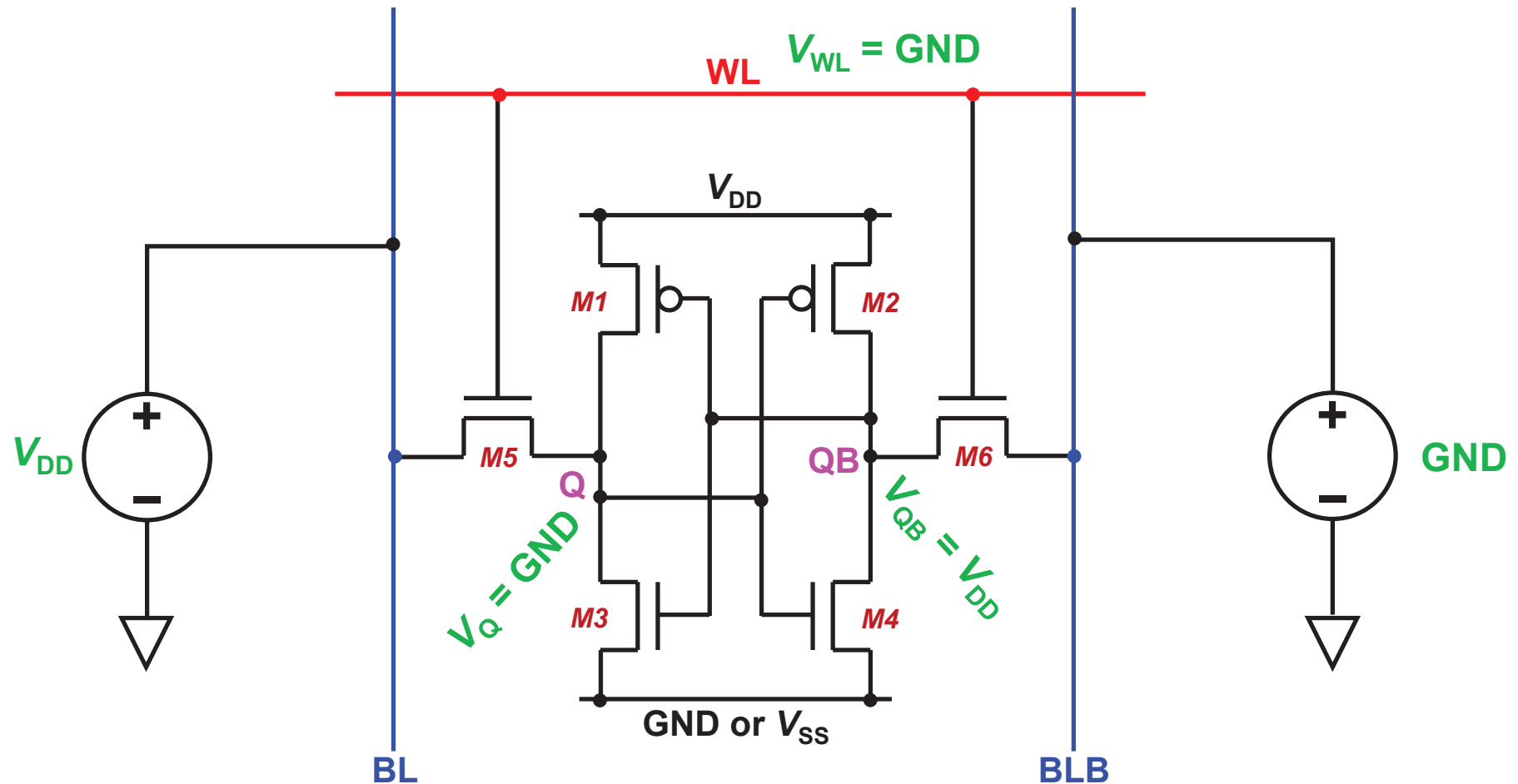
# Writing Data into the 6T SRAM – Put data on BL & BLB



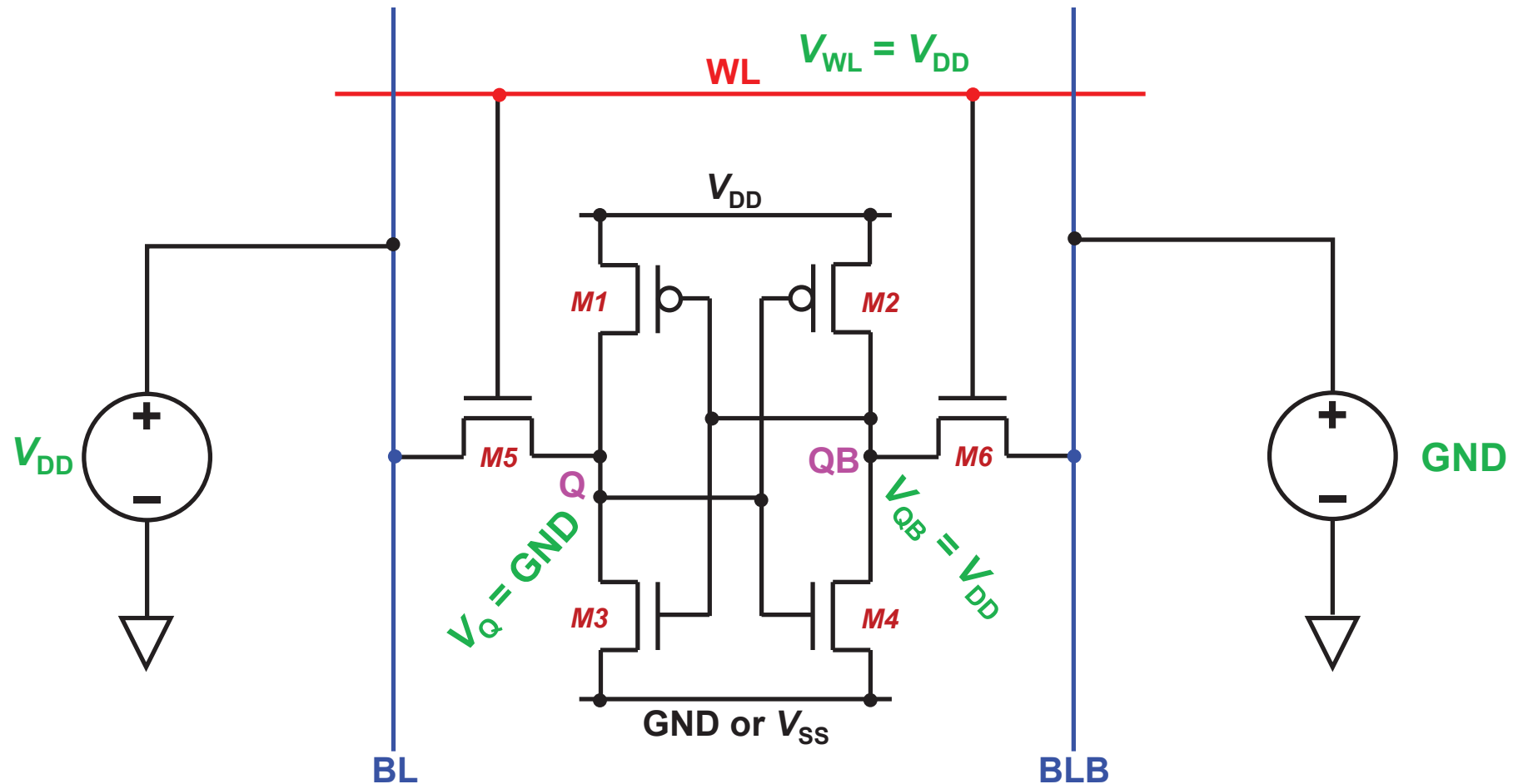
# Writing Data into the 6T SRAM – Turn On WL


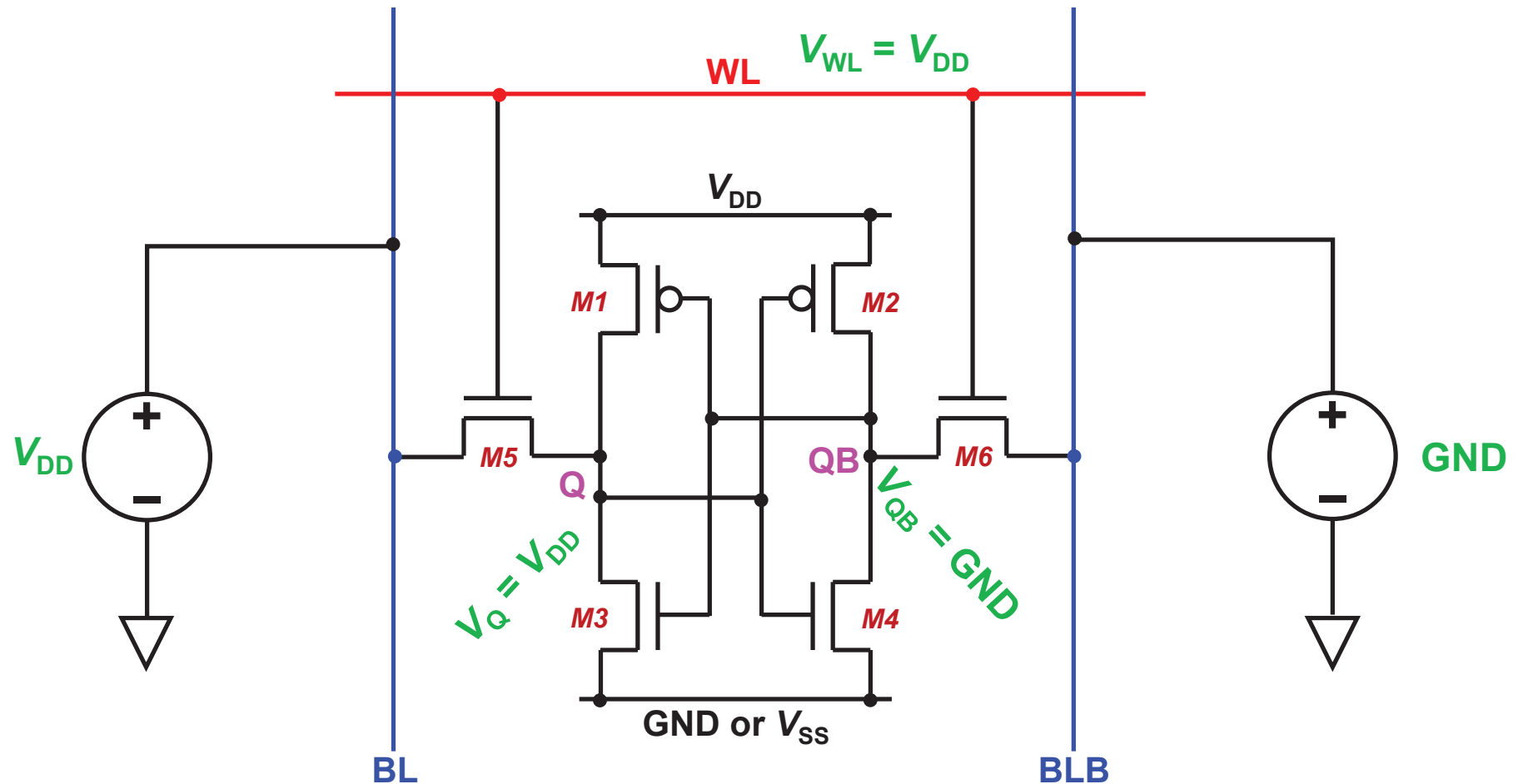
# Writing Data into the 6T SRAM – Turn On WL



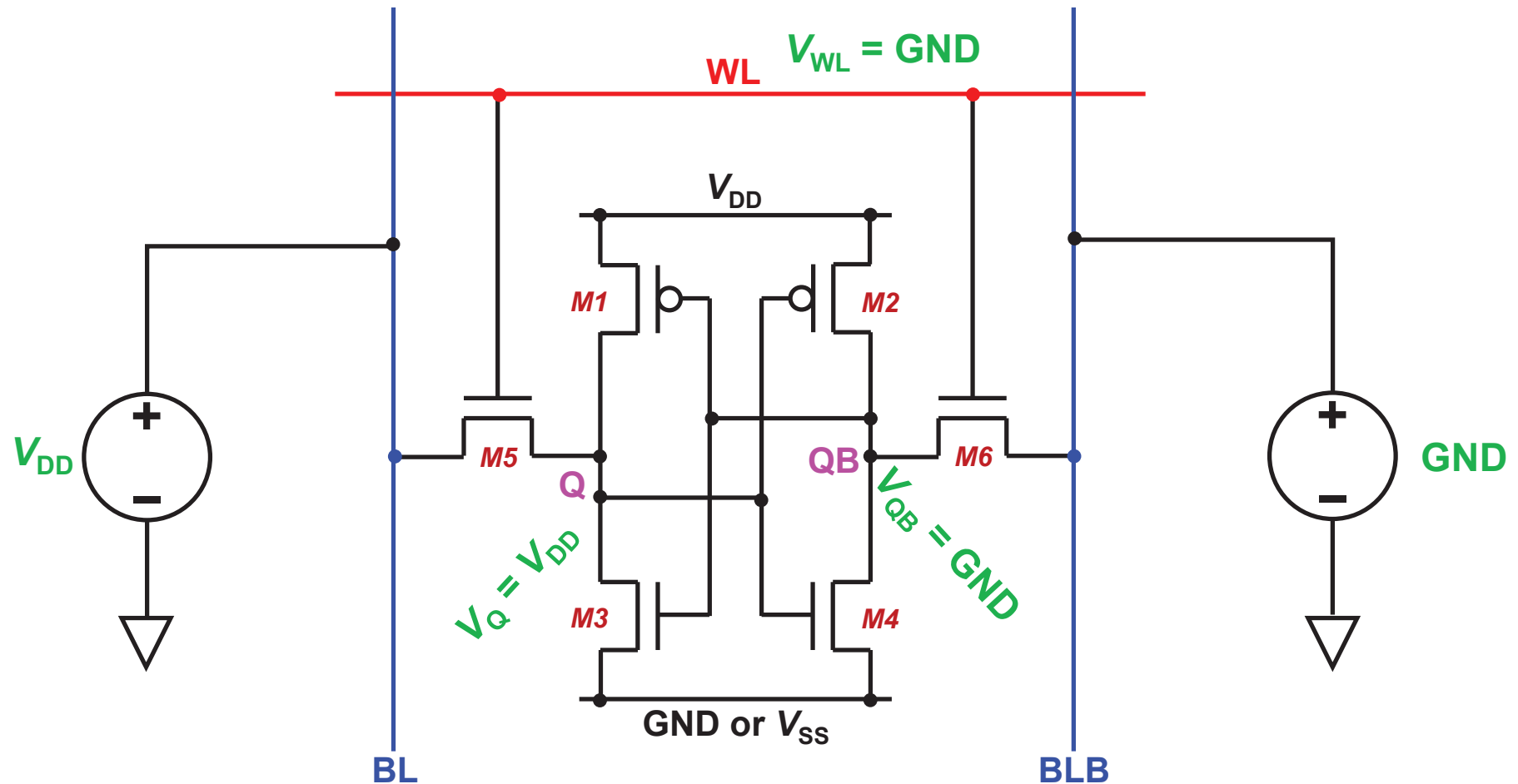
# Writing Data into the 6T SRAM – Turn Off WL









# Reading Data from the 6T SRAM

 

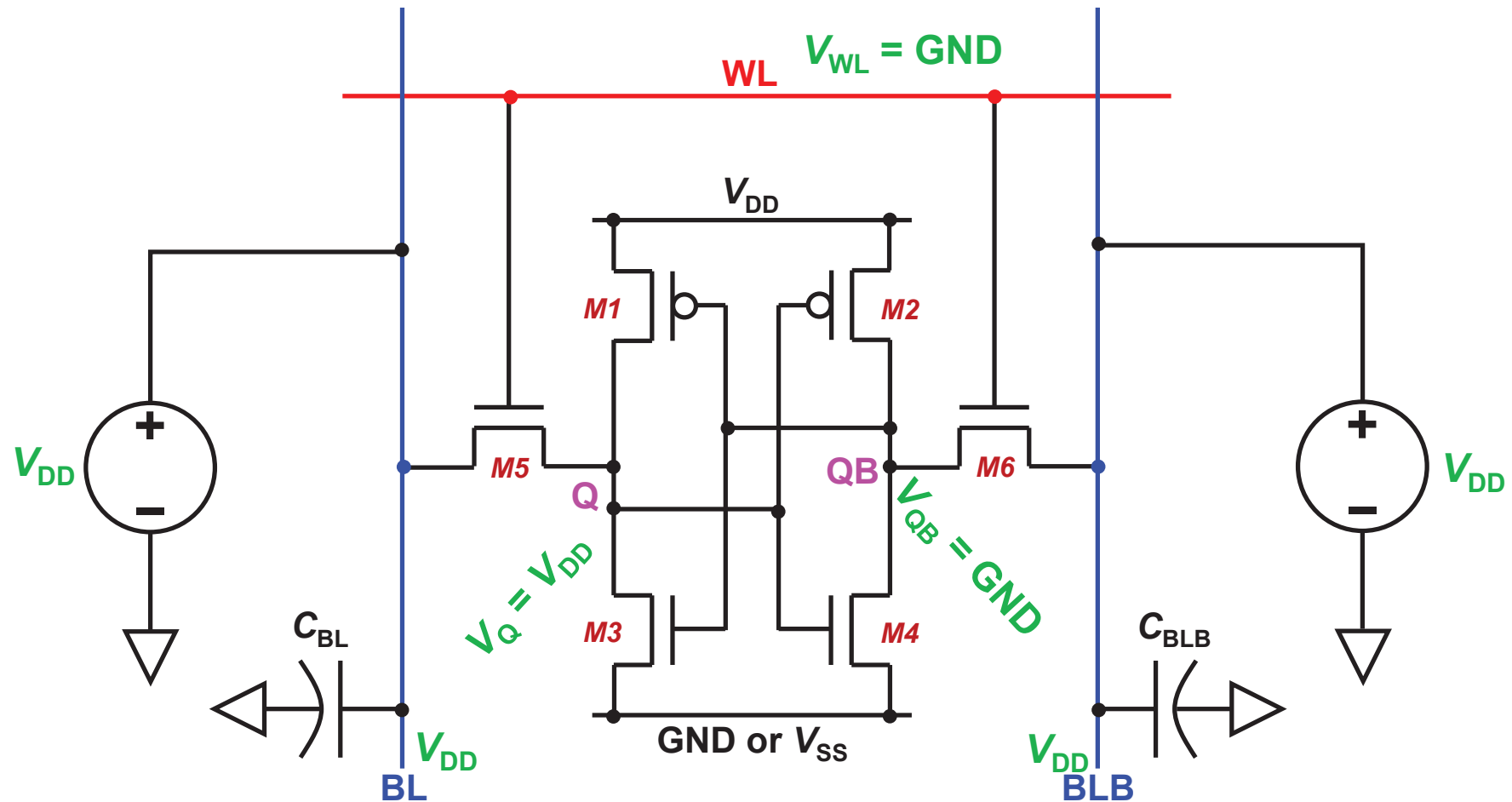
# Reading Data from the 6T SRAM – Precharge BL & BLB



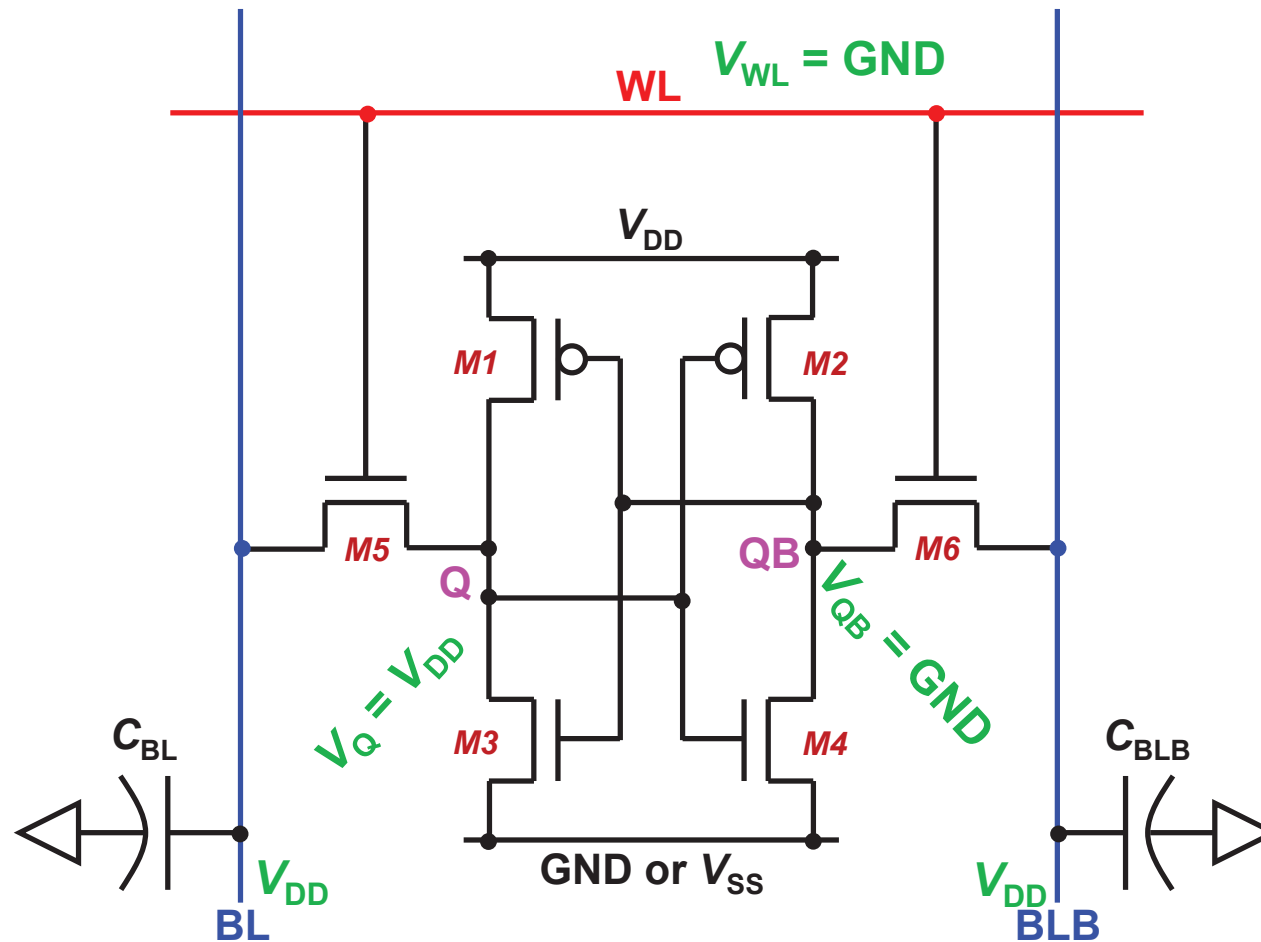
# Reading Data from the 6T SRAM – Precharge BL & BLB



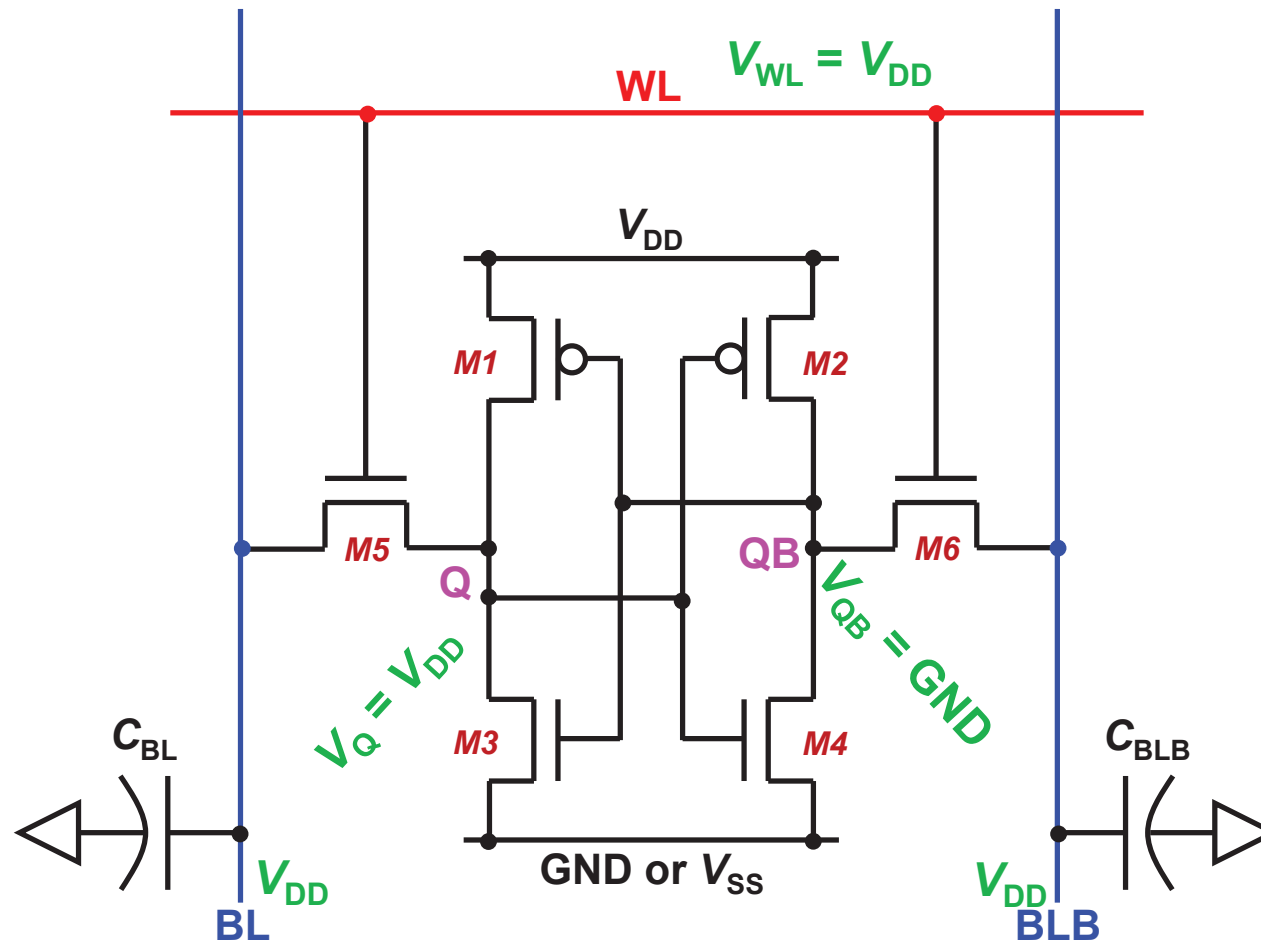
# Reading Data from the 6T SRAM – Turn On WL



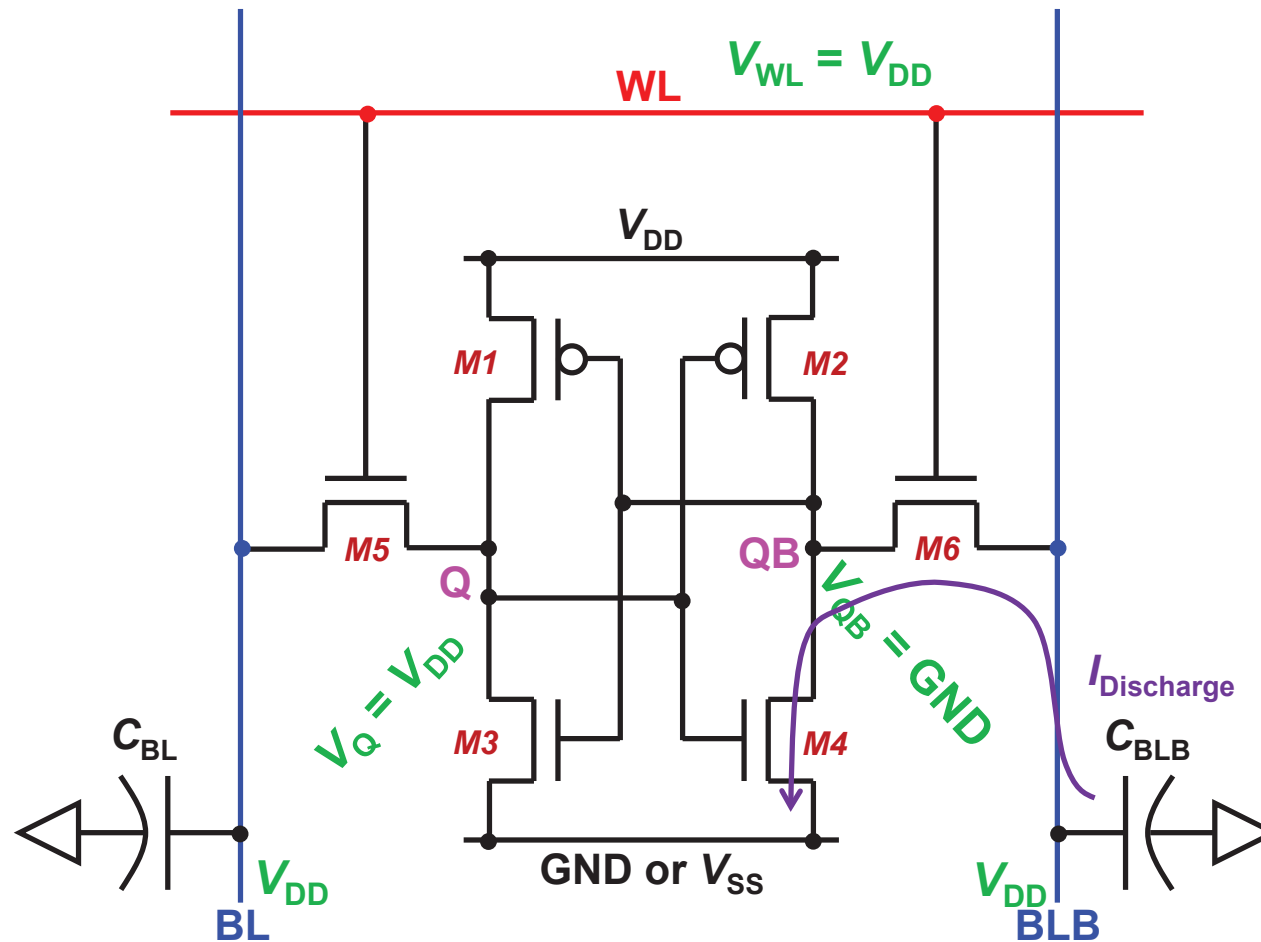
# Reading Data from the 6T SRAM – Discharge BL/BLB


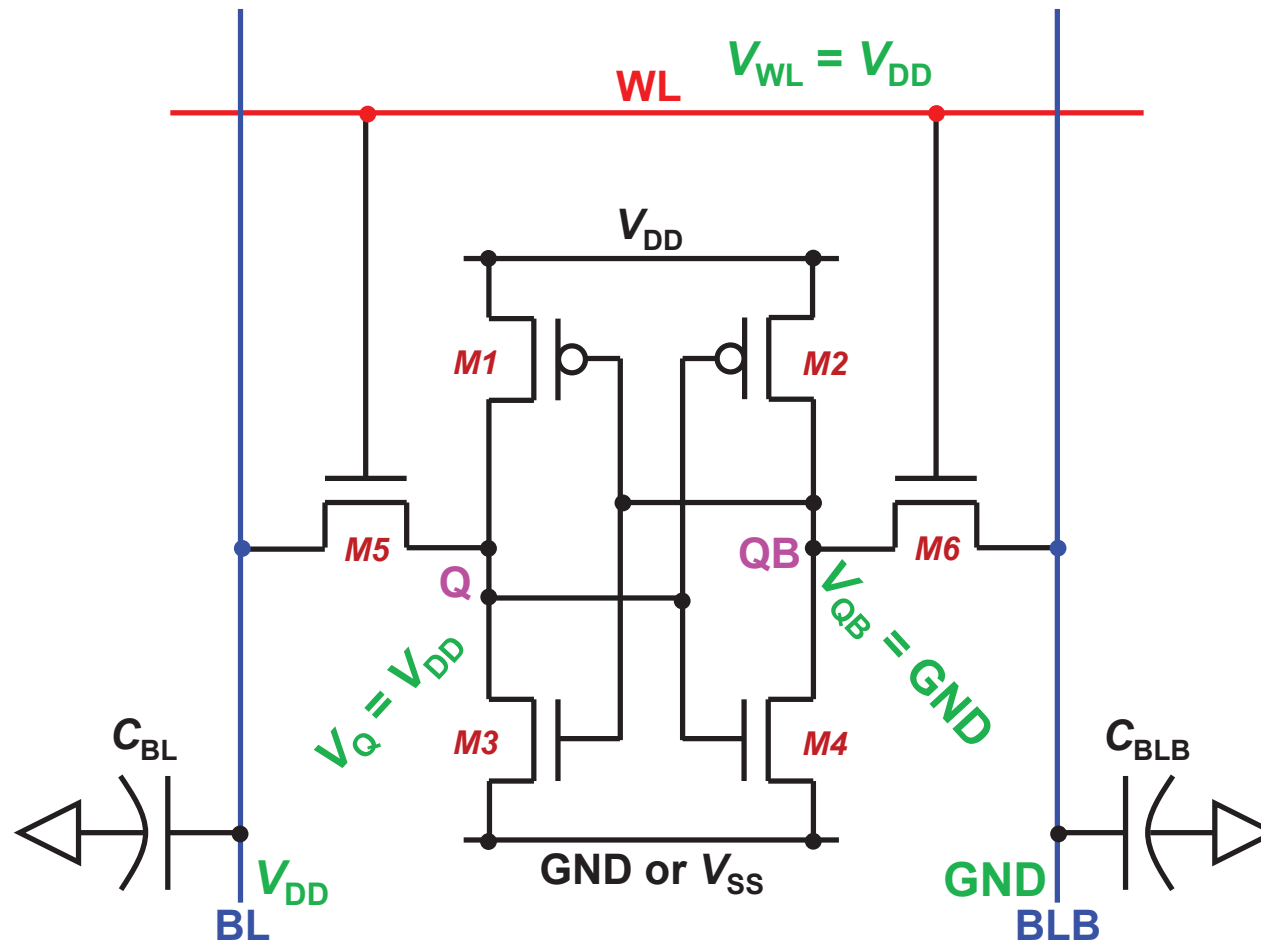
# Reading Data from the 6T SRAM – Sense BL & BLB


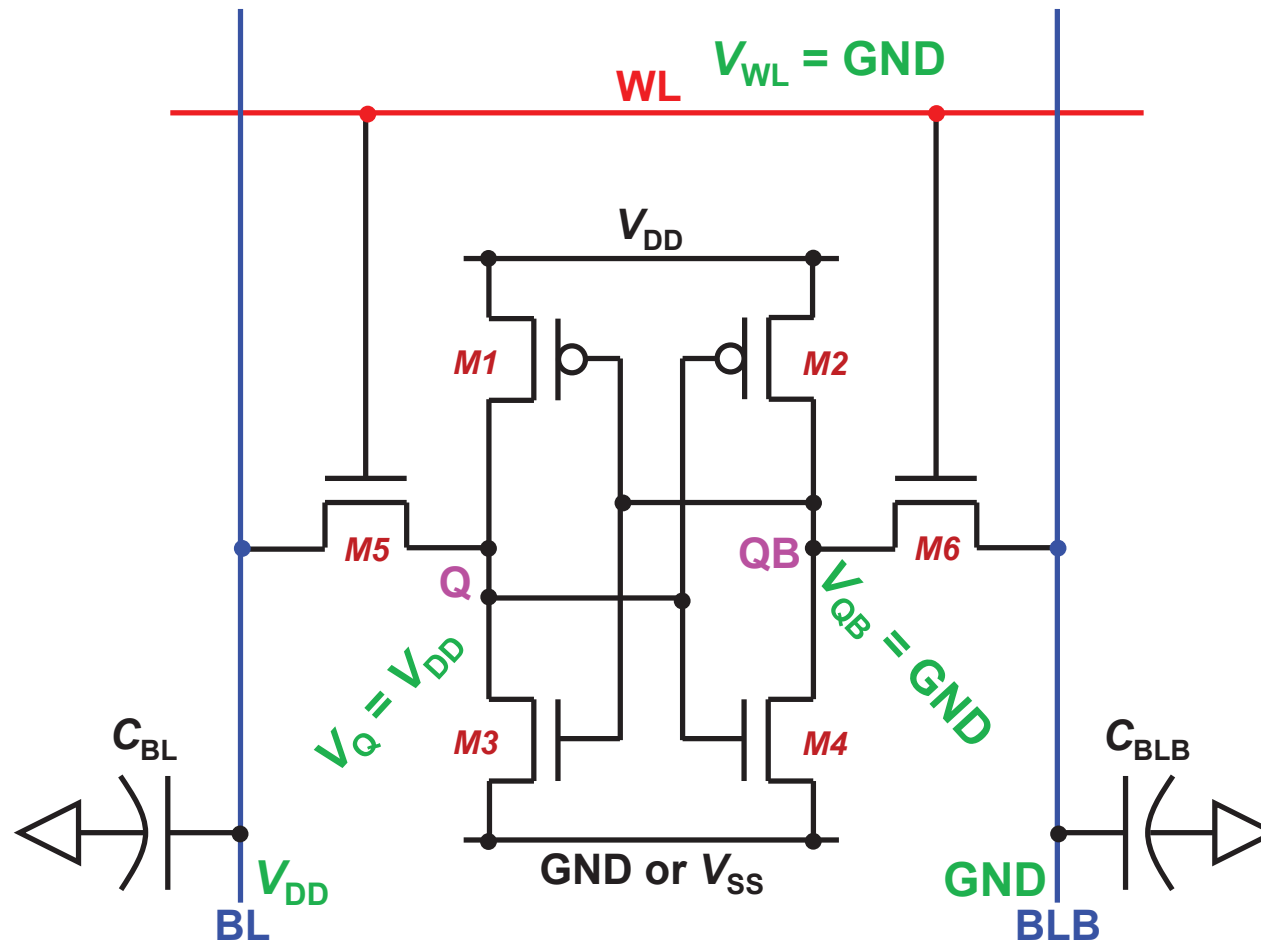
# Reading Data from the 6T SRAM – Turn Off WL




# Week 5-4


Sizing Transistors in SRAM Bit-cell




# Writing Data into the 6T SRAM

 


# Writing Data into the 6T SRAM

 
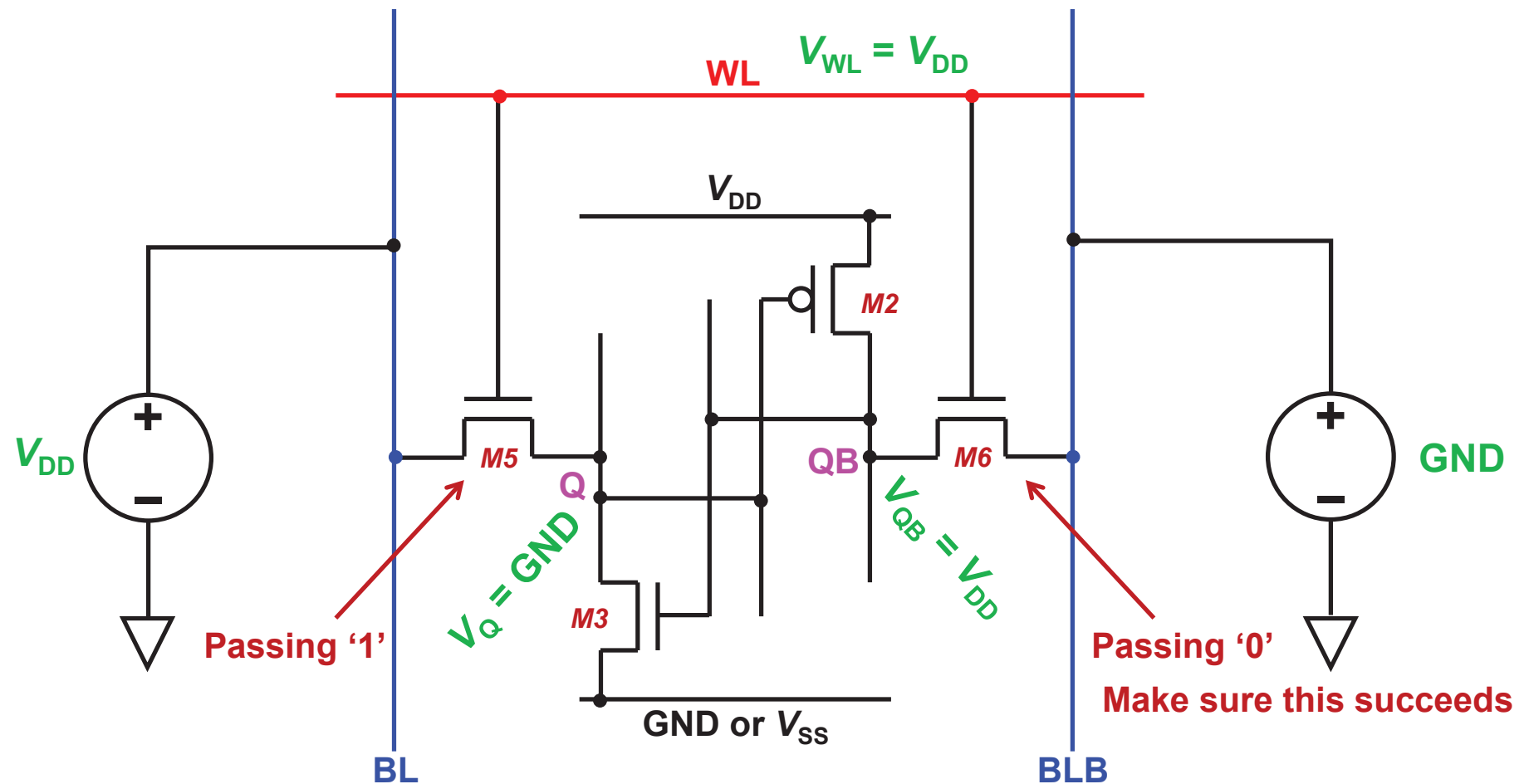
# Writing Data into the 6T SRAM – Half-cell Analysis



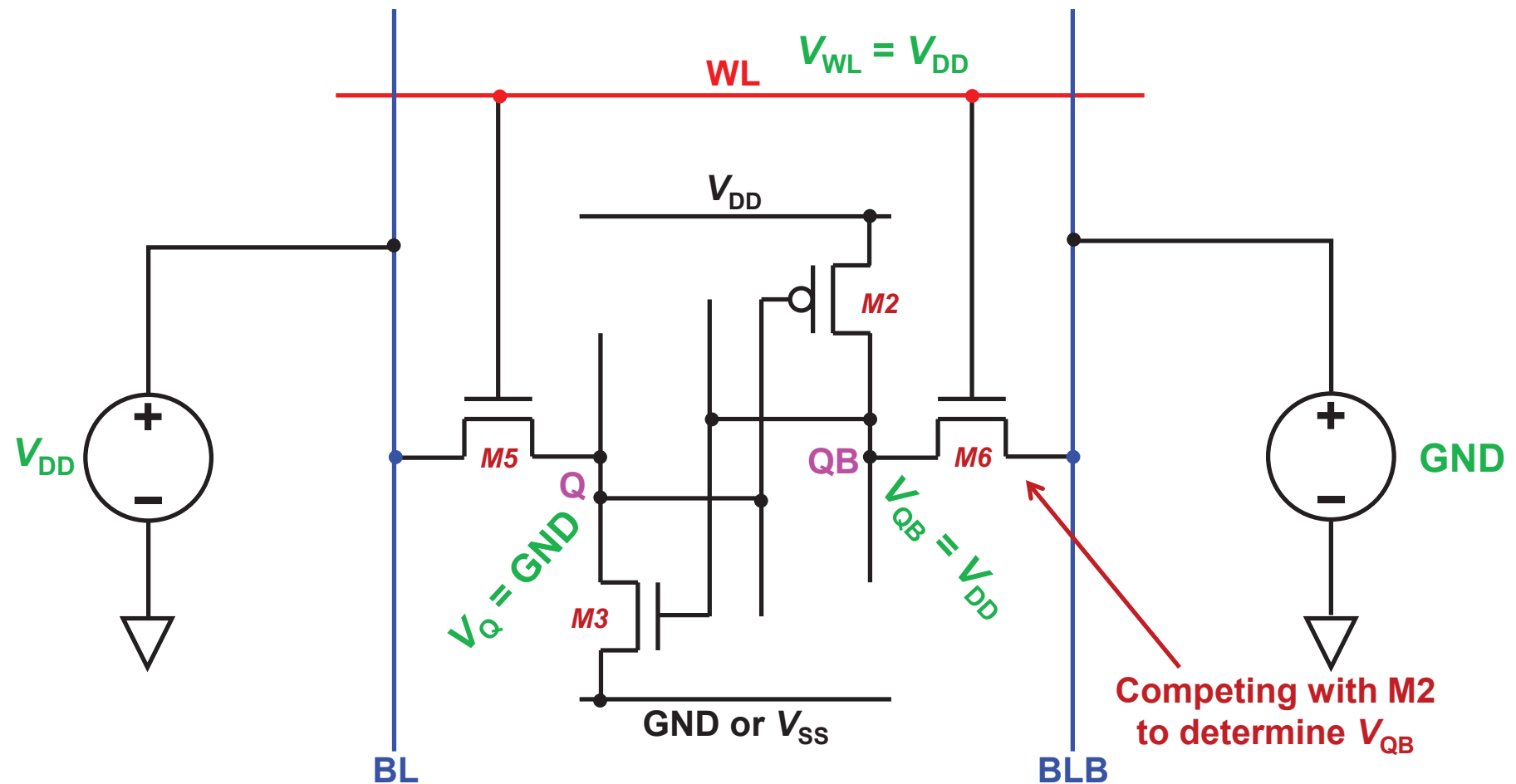
# Writing Data into the 6T SRAM – Half-cell Analysis



**Pull-up Ratio**  $[(W_2/L_2) / (W_6/L_6)]$  determines if  $V_{QB}$  will fall below  $V_M$  of inverter (lower is better)
 
# Impact of Pull-up Ratio on Write Operation of 6T SRAM



PR < 1.8 to ensure write of “0”  
(otherwise, M3 stays on and we cannot write “0” into QB)


$$k_{n,M6} \left( (V_{DD} - V_{TN})V_{QB} - \frac{V_{QB}^2}{2} \right) = k_{p,M2} \left( (V_{TP} - V_{DD})V_{DS,SATp} - \frac{V_{DS,SATp}^2}{2} \right)$$

$$V_{QB} = V_{DD} - V_{TN} - \sqrt{(V_{DD} - V_{TN})^2 - 2 \frac{\mu_p}{\mu_n} \left( (V_{TP} - V_{DD})V_{DS,SATp} - \frac{V_{DS,SATp}^2}{2} \right) PR}$$


$$PR = \frac{W_2/L_2}{W_6/L_6}$$

Want smaller aspect ratio for  $M1$  &  $M2$   
Want larger aspect ratio for  $M5$  &  $M6$


# Reading Data from the 6T SRAM

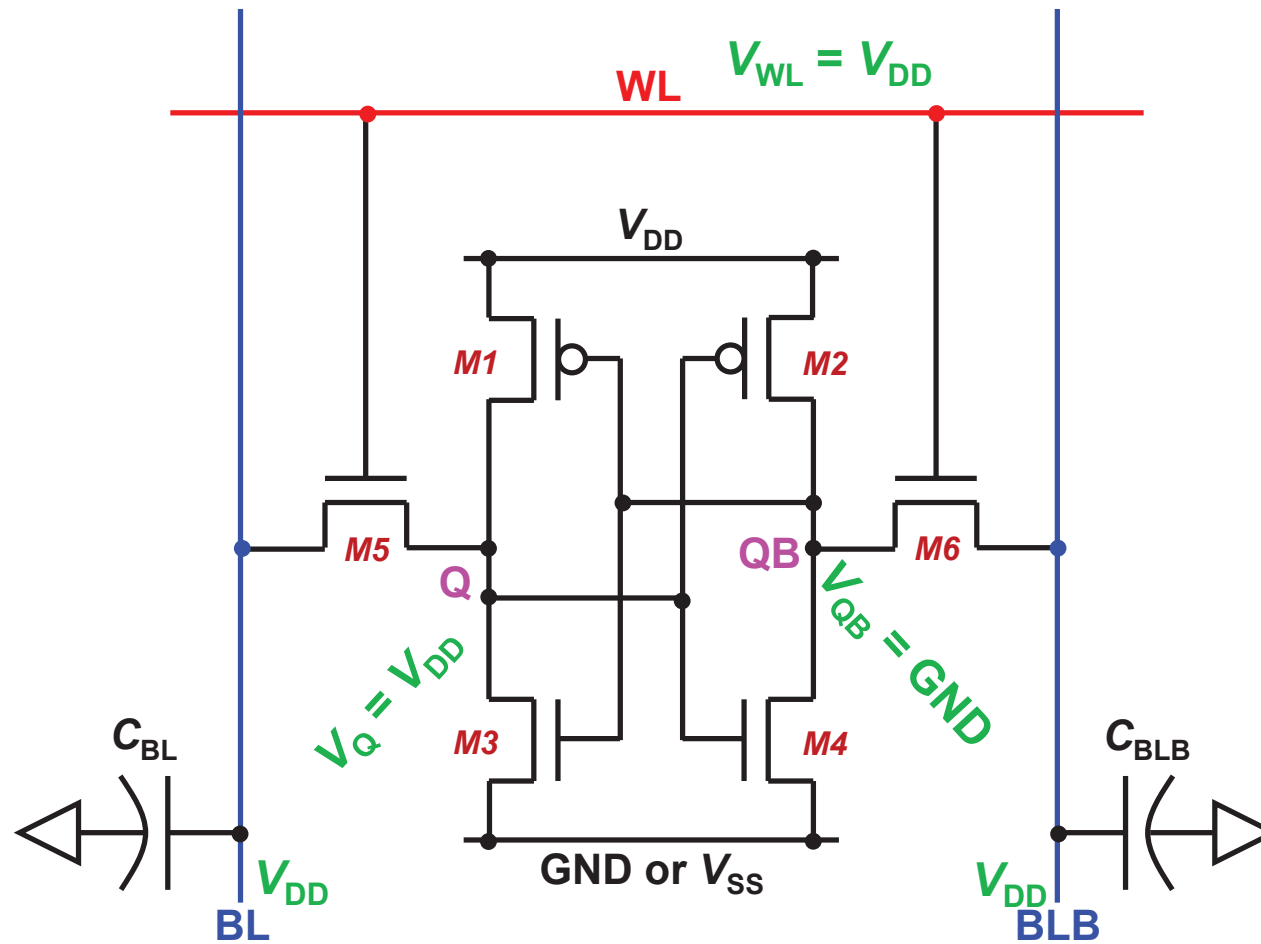

# Reading Data from the 6T SRAM

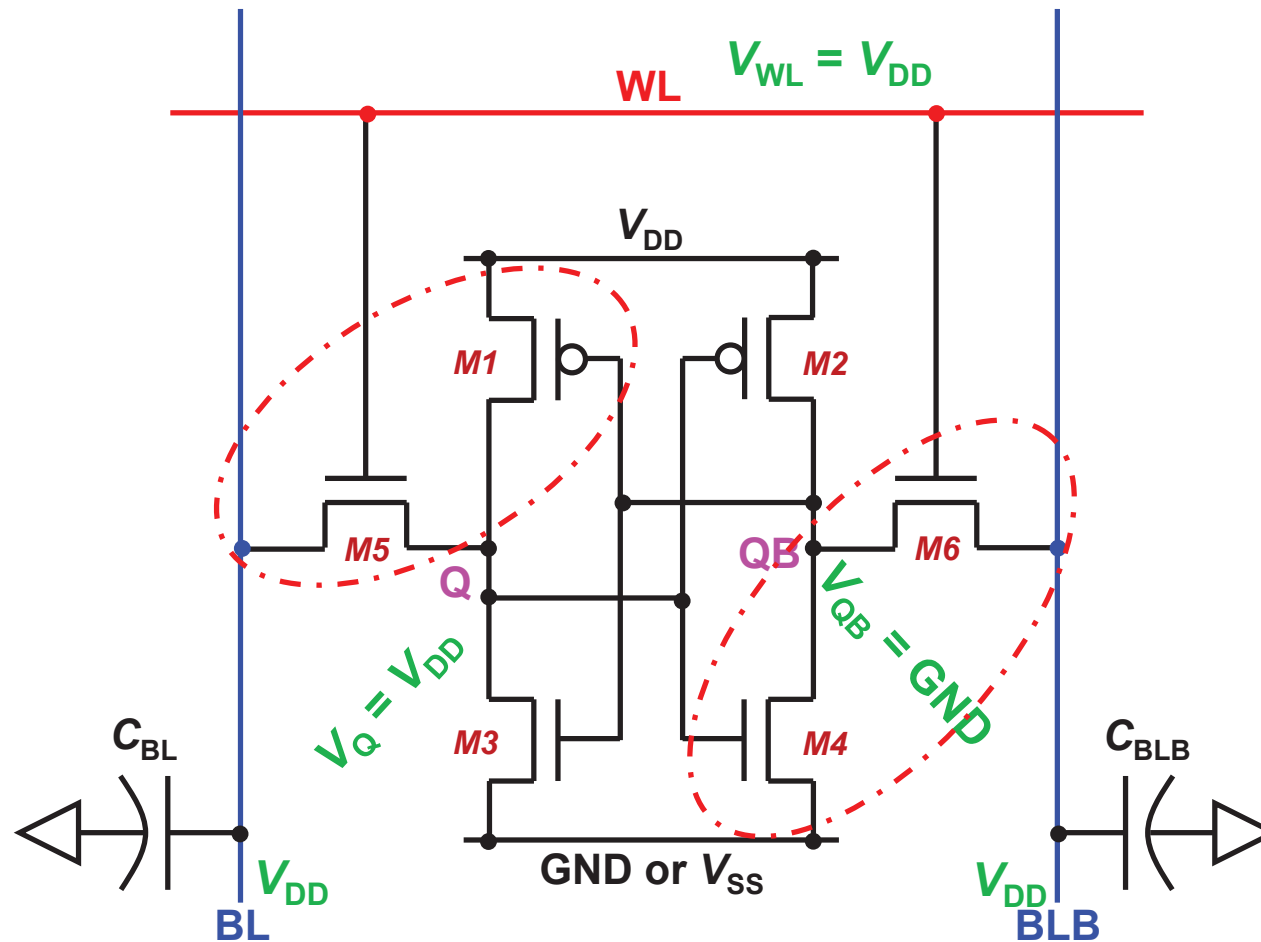
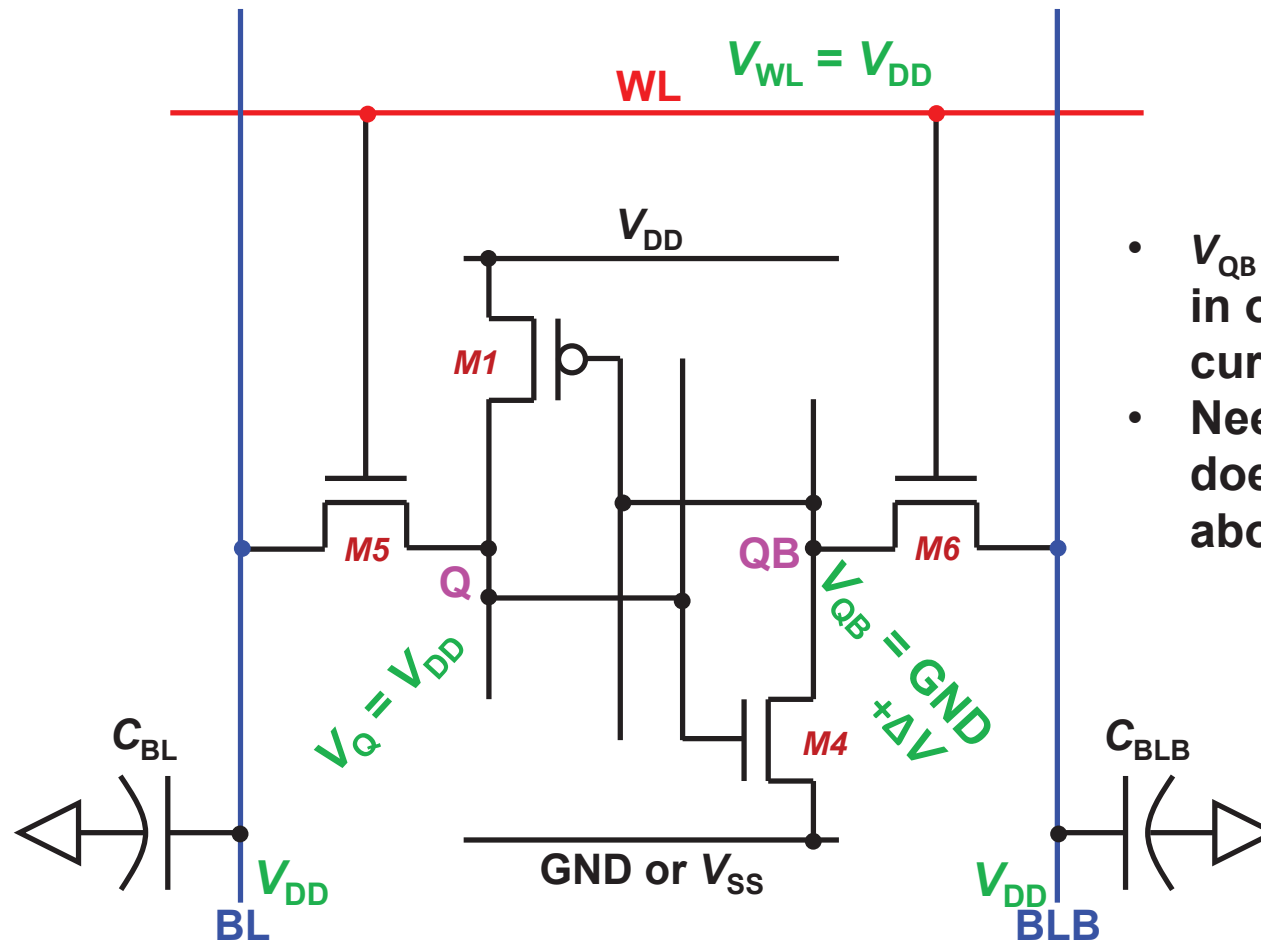
# Reading Data from the 6T SRAM – Half-cell Analysis




- $V_{QB}$  will increase by  $+\Delta V$  in order for M4 to pass current
- Need to ensure  $V_{QB}$  does not increase above  $V_M$  of inverter

Cell Ratio  $[(W_4/L_4) / (W_6/L_6)]$  determines  $+\Delta V$  on  $V_{QB}$  (larger is better)


 
# Impact of Cell Ratio on Read Operation of 6T SRAM



CR > 1.2 to ensure read stability  
(otherwise, bit flip occurs while read operation)

$$k_{n,M6} \left( (V_{DD} - \Delta V - V_{TN}) V_{DS,SATn} - \frac{V_{DS,SATn}^2}{2} \right) = k_{n,M6} \left( (V_{DD} - V_{TN}) \Delta V - \frac{\Delta V^2}{2} \right)$$

$$\Delta V = \frac{V_{DS,SATn}}{CR} + CR(V_{DD} - V_{TN}) - \frac{\sqrt{V_{DS,SATn}^2(1 + CR) + CR^2(V_{DD} - V_{TN})^2}}{CR}$$


$$CR = \frac{W_4/L_4}{W_6/L_6}$$

Want larger aspect ratio for  $M3$  &  $M4$   
Want smaller aspect ratio for  $M5$  &  $M6$

# Week 5-5


Introduction to the 1-Transistor Dynamic RAM (1T DRAM)
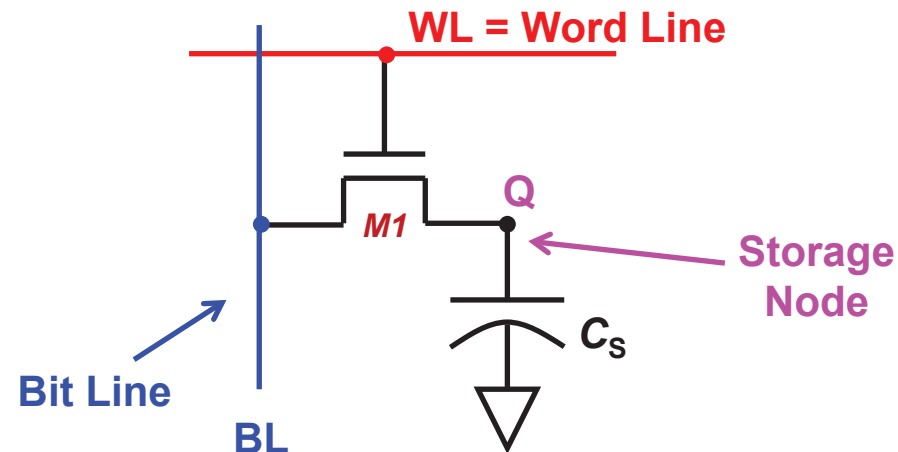
# The 1-Transistor Dynamic RAM (1T DRAM) Bitcell




- Unlike SRAM
  - The 1T DRAM cell has only one transistor and one capacitor
  - Single-ended
- Simple structure and compact in size (good for density)
- Data is stored as the amount of charge in the storage capacitor
- Node Q is in high-**Z** state when  $V_{WL} = \mathbf{GND}$ 
  - Stored charge will leak due to transistor leakage
  - Requires dynamic refresh of charge stored to retain data (hence, *dynamic* RAM)
 
# Array of 1T DRAM Bitcells (Bitcell Array)



# The 1T1R DRAM Bitcell Structure

 


- The bitcell is *accessed* to read data from or write data into the bitcell
  - Electrically connect BL to storage node Q
- Otherwise, bitcell is in hold or hold mode and retains its stored data
  - Affected by leakage
  - Higher  $C_s$  allows more charge to be stored
    - Longer data retention

# Week 5-6


DRAM Read and Write Operations

# The 1T1C DRAM

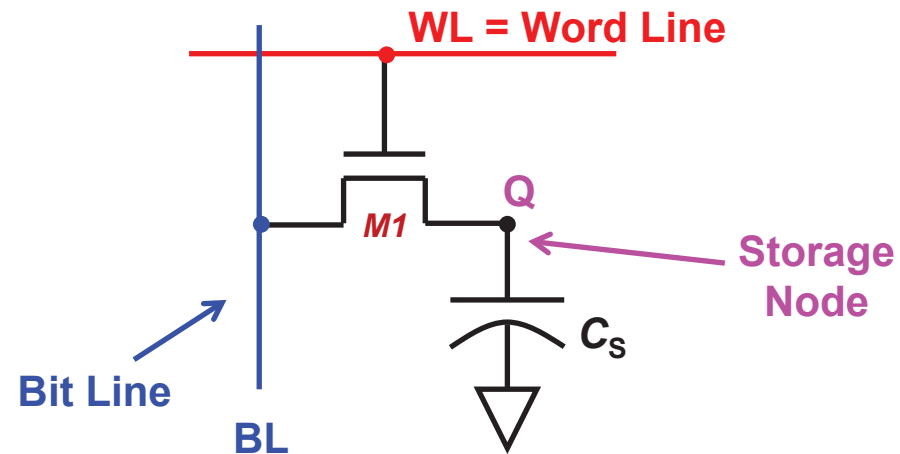

- Unlike SRAM
  - The 1T DRAM cell has only one transistor and one capacitor
  - Single-ended
- Simple structure and compact in size (good for density)
- Data is stored as the amount of charge in the storage capacitor
- Node Q is in high-**Z** state when  $V_{WL} = \mathbf{GND}$ 
  - Stored charge will leak due to transistor leakage
  - Requires dynamic refresh of charge stored to retain data (hence, *dynamic* RAM)

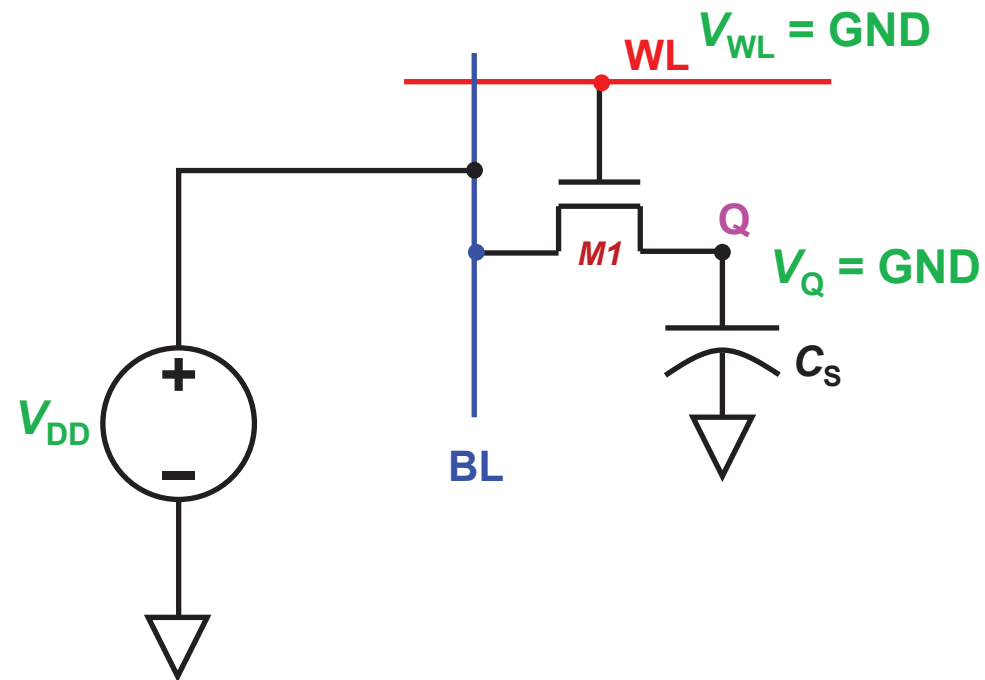
# Writing Data into the 1T 1R DRAM – Put data on BL








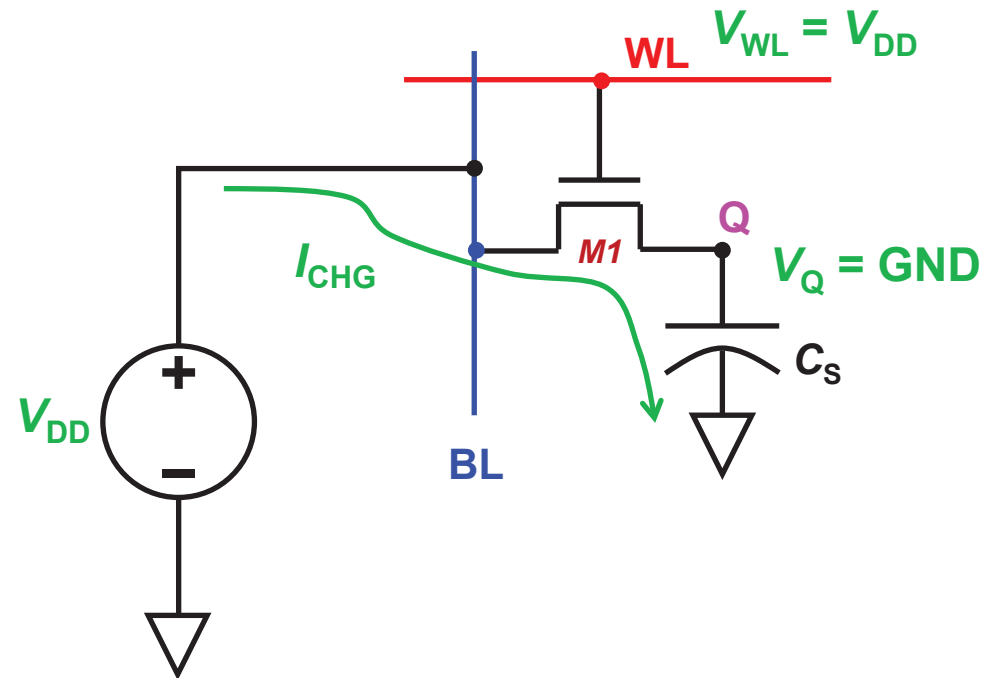
# Writing Data into the 1T DRAM – Turn on WL



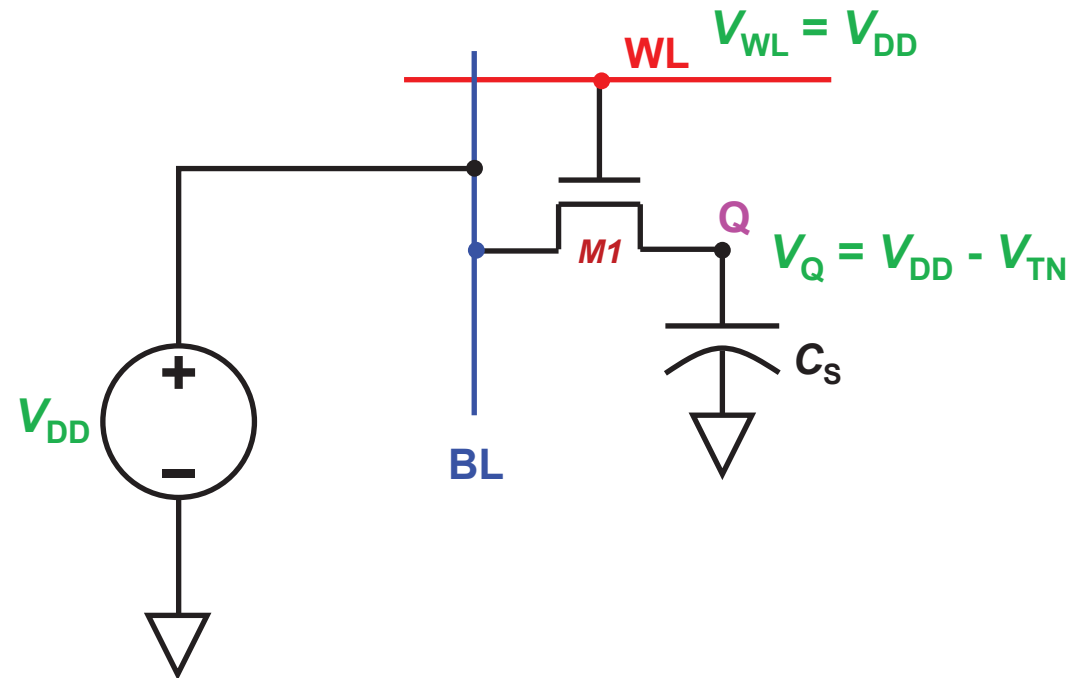
# Writing Data into the 1T 1R DRAM – Turn on WL



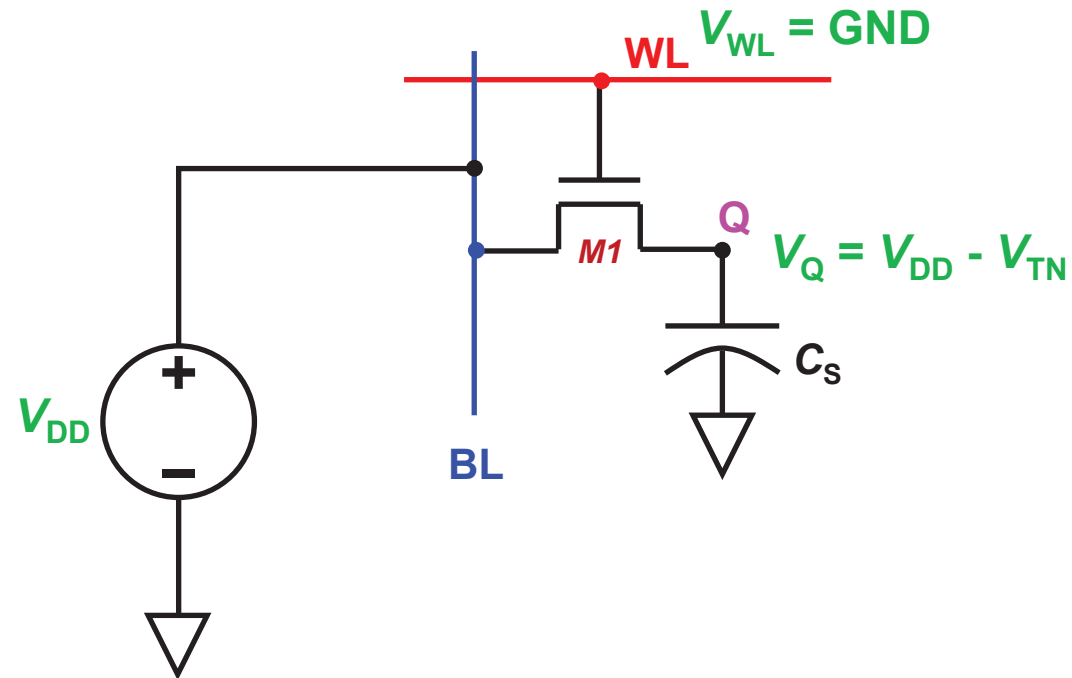
# Writing Data into the 1T 1R DRAM – Turn off WL



 
# Writing Data into the 1T DRAM – Disconnect BL



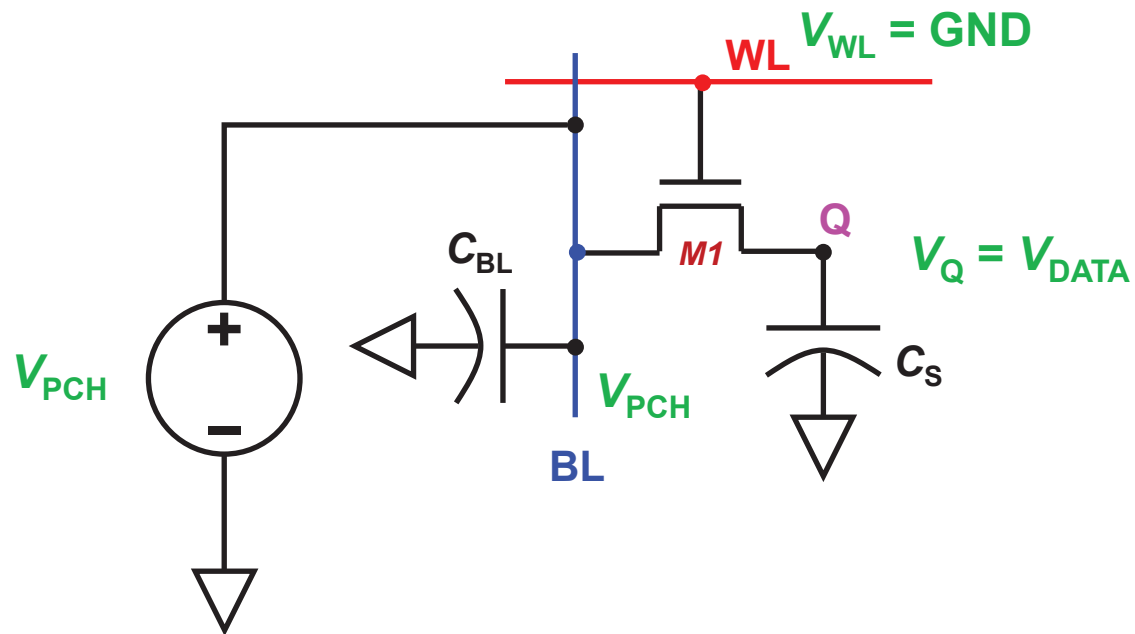
# Reading Data from the 1T DRAM – Precharge BL


 
# Reading Data from the 1T DRAM – Precharge BL



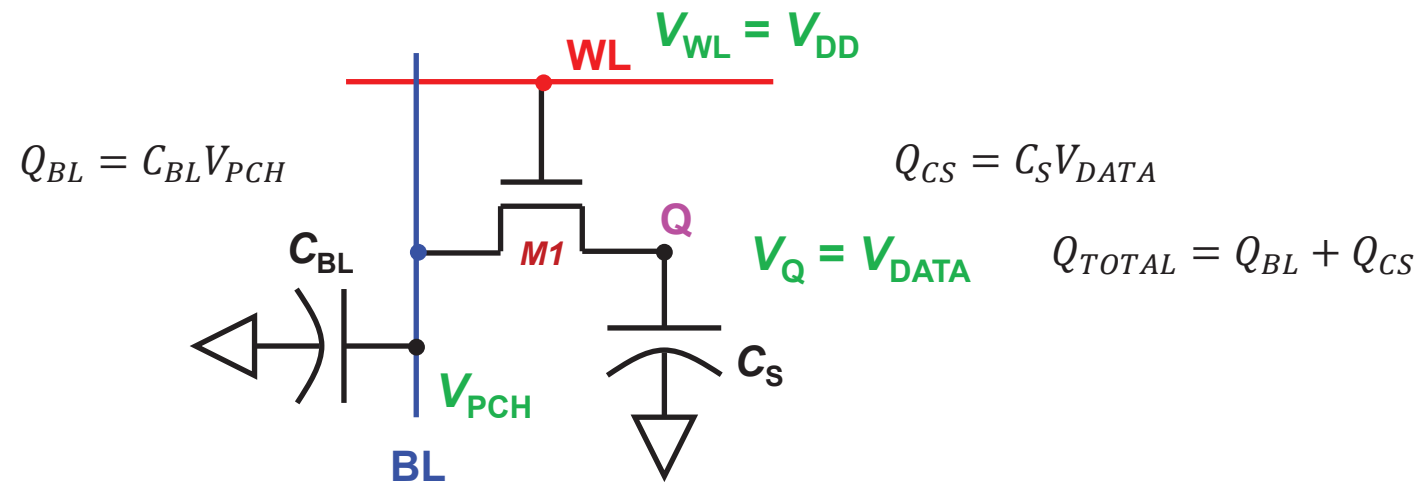
# Reading Data from the 1T DRAM – Turn on WL



- M1 electrically shorts C<sub>BL</sub> and C<sub>S</sub> together
  - Charge sharing between C<sub>BL</sub> and C<sub>S</sub>
  - $\Delta V_Q$  and  $\Delta V_{BL}$  depends on size of C<sub>BL</sub> relative C<sub>S</sub>, and whether M1 gets turned off or not



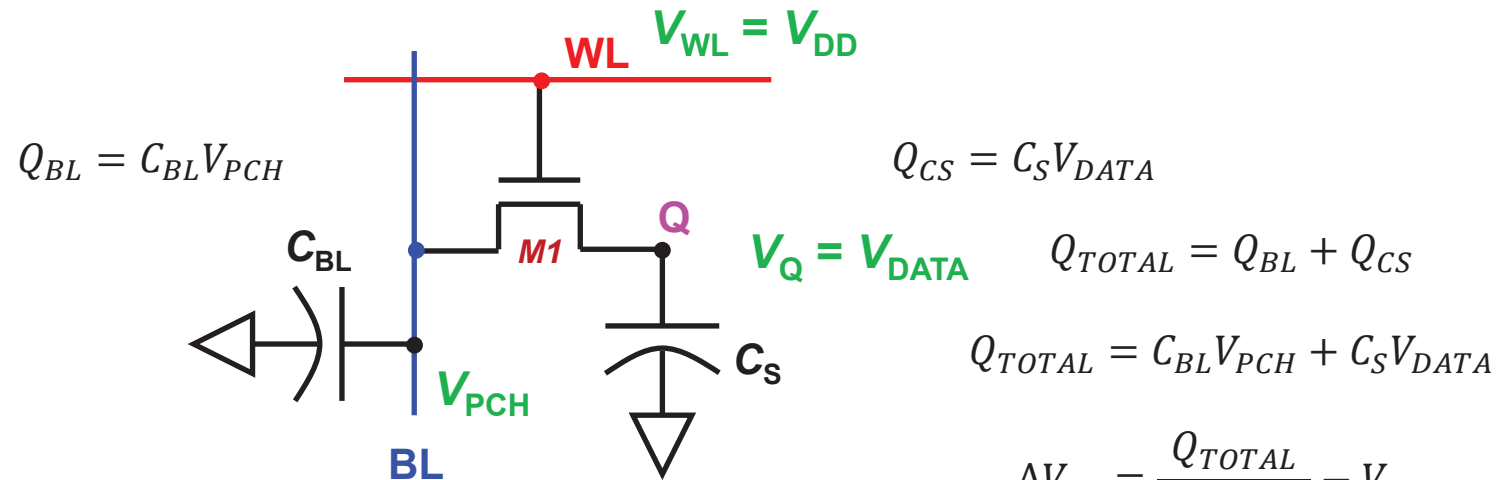
# Reading Data from the 1T DRAM – Turn on WL




- M1 electrically shorts  $C_{BL}$  and  $C_S$  together
  - Charge sharing between  $C_{BL}$  and  $C_S$
  - $\Delta V_Q$  and  $\Delta V_{BL}$  depends on size of  $C_{BL}$  relative  $C_S$ , and whether M1 gets turned off or not
 
# Reading Data from the 1T DRAM – Sense BL




- Use inverter chain to sense logic value on bit-line
  - NMOS pass gate prevents writing back during sensing
 
# Reading Data from the 1T DRAM – Writeback into Cell




- Use inverter chain to sense logic value on bit-line
  - NMOS pass gate prevents writing back during sensing
  - Pass gate activates after sensing to write sensed data back into the cell
 
# Reading Data from the 1T DRAM – Turn off WL



- Use inverter chain to sense logic value on bit-line
  - NMOS pass gate prevents writing back during sensing
  - Pass gate activates after sensing to write sensed data back into the cell
 
# Reading Data from the 1T DRAM – Turn off Pass Gate




- Use inverter chain to sense logic value on bit-line
  - NMOS pass gate prevents writing back during sensing
  - Pass gate activates after sensing to write sensed data back into the cell


# Week 5-7

Introduction to Flash Memory

# MOS Memory Classification

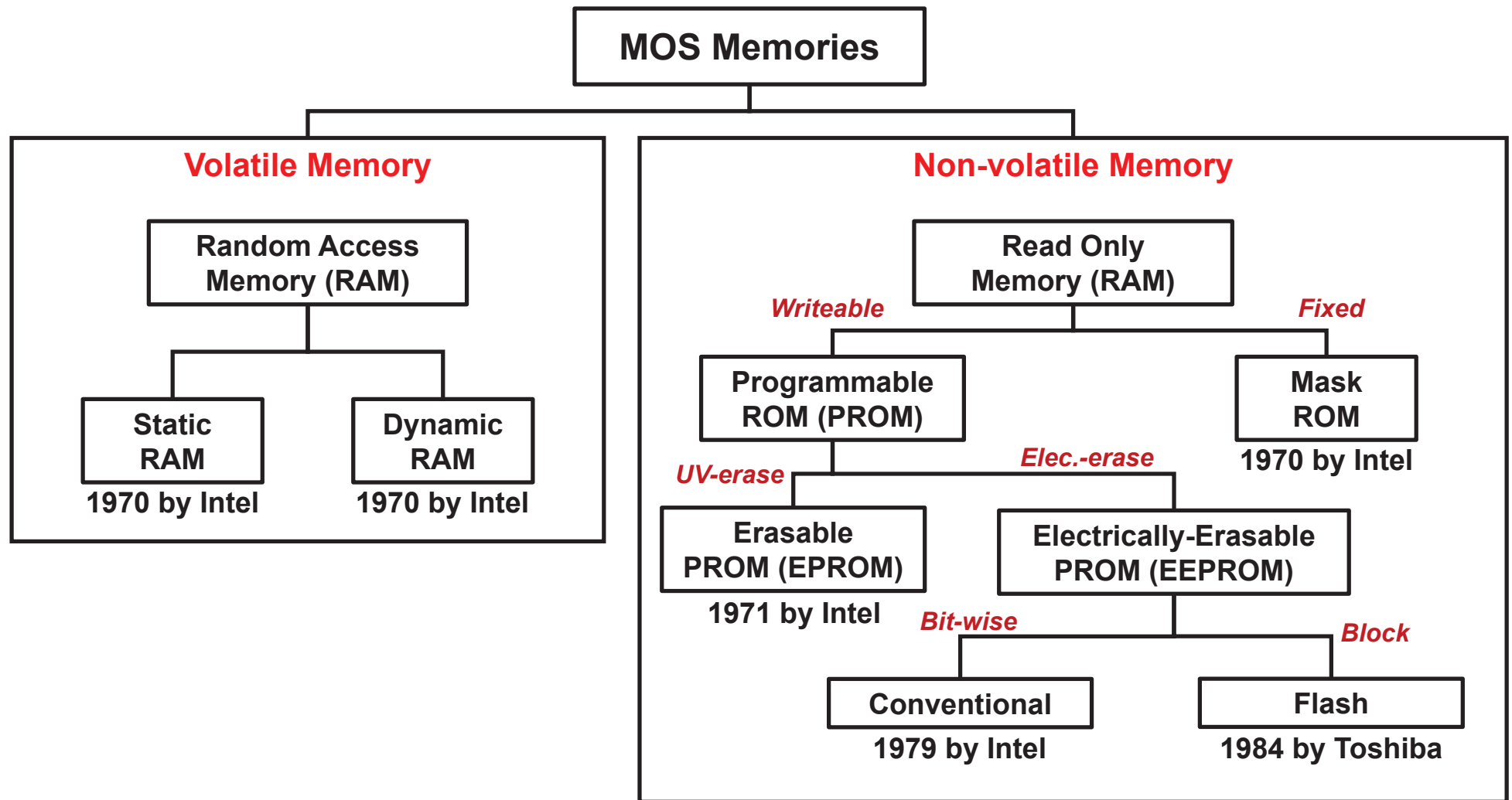

 
# The Floating Gate Field-effect Transistor (FET)



- Floating gate is embedded in oxide between control gate and channel region
- Control gate, source, drain and body terminals are connected to rest of circuit
- Control gate used like gate of an FET
- Charge can be stored in floating gate and sensed as change in threshold voltage,  $V_{TH}$ , of the FET



 
# The Floating Gate Field-effect Transistor (FET)




- Charges added to control gate must be balanced by charges in substrate AND floating gate so that overall charge is zero (charge neutrality)
- Charges on floating gate shields substrate from electric field charges on control gate, which then changes the threshold voltage,  $V_{TH}$ , of the transistor
 
# Flash Memory Based on Floating Gate FET




# Flash Memory Based on Floating Gate FET

## Architecture of NAND Flash

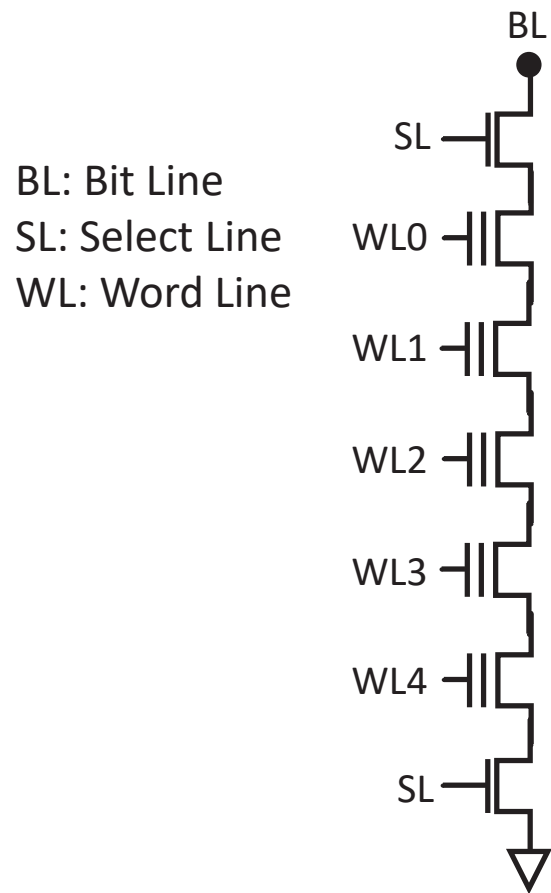


# Flash Memory Based on Floating Gate FET

## Architecture of NAND Flash

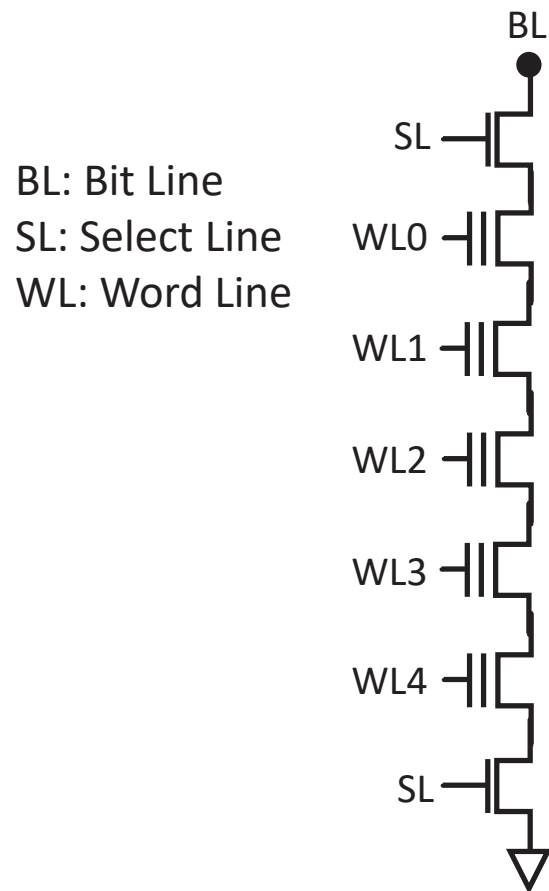


## Architecture of NOR Flash

 

 
# Read Operations in NAND Flash

BL: Bit Line  
SL: Select Line  
WL: Word Line


 
# Read Operations in NAND Flash


BL: Bit Line  
SL: Select Line  
WL: Word Line



- Step #1: Charge BL to voltage  $V_{BL}$   
 Step #2: Apply voltage  $V_{WL}$  to all WLs except the WL being connected to the selected bitcell
- FETs with high  $V_{TH}$  are ON
  - State of selected FET depends on  $V_{TH}$  due to stored charge
 
# Read Operations in NAND Flash

BL: Bit Line  
SL: Select Line  
WL: Word Line



Step #1: Charge BL to voltage  $V_{BL}$   
Step #2: Apply voltage  $V_{WL}$  to all WLs except the WL being connected to the selected bitcell


- FETs with high  $V_{TH}$  are ON
- State of selected FET depends on  $V_{TH}$  due to stored charge

Step #3: Apply voltage,  $V_{SL}$ , to SL

- Allow possible path to discharge  $C_{BL}$  through the NAND string
- Depends on whether selected FET is ON or OFF
  - ON:  $V_{BL} \rightarrow GND$
 
# Read Operations in NAND Flash

BL: Bit Line  
SL: Select Line  
WL: Word Line



Step #1: Charge BL to voltage  $V_{BL}$

Step #2: Apply voltage  $V_{WL}$  to all WLs except the WL being connected to the selected bitcell

- FETs with high  $V_{TH}$  are ON
- State of selected FET depends on  $V_{TH}$  due to stored charge

Step #3: Apply voltage,  $V_{SL}$ , to SL


- Allow possible path to discharge  $C_{BL}$  through the NAND string
- Depends on whether selected FET is ON or OFF
  - ON:  $V_{BL} \rightarrow GND$

Step #4: Ground all WLs and SLs


 
# Read Operations in NAND Flash

BL: Bit Line  
SL: Select Line  
WL: Word Line



Step #1: Charge BL to voltage  $V_{BL}$

Step #2: Apply voltage  $V_{WL}$  to all WLs except the WL being connected to the selected bitcell

- FETs with high  $V_{TH}$  are ON
- State of selected FET depends on  $V_{TH}$  due to stored charge

Step #3: Apply voltage,  $V_{SL}$ , to SL

- Allow possible path to discharge  $C_{BL}$  through the NAND string
- Depends on whether selected FET is ON or OFF
  - ON:  $V_{BL} \rightarrow GND$

Step #4: Ground all WLs and SLs


Step #5: Sense voltage of BL

# Write Operations in NAND Flash

BL: Bit Line  
SL: Select Line  
WL: Word Line

High resistance path between CG to substrate through the FG due to insulating oxide

 Large electric field can force tunneling current to flow by Fowler-Nordheim (FN) tunneling mechanism



Main idea: drive current between CG and substrate for a short period of time. Charges get trapped on the FG when current is abruptly turned off


# Write Operations in NAND Flash

BL: Bit Line  
SL: Select Line  
WL: Word Line

High resistance path between CG to substrate through the FG due to insulating oxide

Large electric field can force tunneling current to flow by Fowler-Nordheim (FN) tunneling mechanism

 Constraint: no negative voltage allowed  
(difficult to generate)



Main idea: drive current between CG and substrate for a short period of time. Charges get trapped on the FG when current is abruptly turned off


# Write Operations in NAND Flash

BL: Bit Line  
SL: Select Line  
WL: Word Line

High resistance path between CG to substrate through the FG due to insulating oxide

Large electric field can force tunneling current to flow by Fowler-Nordheim (FN) tunneling mechanism

 Constraint: no negative voltage allowed  
(difficult to generate)



Main idea: drive current between CG and substrate for a short period of time. Charges get trapped on the FG when current is abruptly turned off

PROGRAM operation:

- Set voltage of substrate voltage to *GND*
- Apply programming voltage ( $V_{PRG}$ ) to selected bitcell to drive current,  $I_{PRG}$


# Write Operations in NAND Flash

BL: Bit Line  
SL: Select Line  
WL: Word Line

High resistance path between CG to substrate through the FG due to insulating oxide

Large electric field can force tunneling current to flow by Fowler-Nordheim (FN) tunneling mechanism

 Constraint: no negative voltage allowed  
(difficult to generate)



Main idea: drive current between CG and substrate for a short period of time. Charges get trapped on the FG when current is abruptly turned off

PROGRAM operation:


- Set voltage of substrate voltage to *GND*
- Apply programming voltage ( $V_{PRG}$ ) to selected bitcell to drive current,  $I_{PRG}$

(block) ERASE operation:

- Set all WL voltages to *GND*
- Apply erase voltage ( $V_{ERS}$ ) to common substrate to drive current,  $I_{ERS}$ , through all bitcells in the NAND string

 
# Read Operations in NOR Flash

BL: Bit Line  
SL: Select Line  
WL: Word Line


 
# Read Operations in NOR Flash

BL: Bit Line  
SL: Select Line  
WL: Word Line




Step #1: Charge BL to voltage  $V_{BL}$

Step #2: Apply voltage  $V_{WL}$  the WL being connected to the selected bitcell

- Selected FETs with low  $V_{TH}$  are ON
- Allow possible path to discharge  $C_{BL}$  through the selected bitcell
- Whether selected FET is ON or OFF depends on stored charge
  - ON:  $V_{BL} \rightarrow GND$
 
# Read Operations in NOR Flash

BL: Bit Line  
SL: Select Line  
WL: Word Line



Step #1: Charge BL to voltage  $V_{BL}$

Step #2: Apply voltage  $V_{WL}$  the WL being connected to the selected bitcell


- Selected FETs with low  $V_{TH}$  are ON
- Allow possible path to discharge  $C_{BL}$  through the selected bitcell
- Whether selected FET is ON or OFF depends on stored charge
  - ON:  $V_{BL} \rightarrow GND$

Step #3: Ground all WLs


 
# Read Operations in NOR Flash

BL: Bit Line  
SL: Select Line  
WL: Word Line



Step #1: Charge BL to voltage  $V_{BL}$

Step #2: Apply voltage  $V_{WL}$  the WL being connected to the selected bitcell

- Selected FETs with low  $V_{TH}$  are ON
- Allow possible path to discharge  $C_{BL}$  through the selected bitcell
- Whether selected FET is ON or OFF depends on stored charge
  - ON:  $V_{BL} \rightarrow GND$

Step #3: Ground all WLs


Step #4: Sense voltage of BL

# Write Operations in NOR Flash

BL: Bit Line  
SL: Select Line  
WL: Word Line

High resistance path between CG to substrate through the FG due to insulating oxide

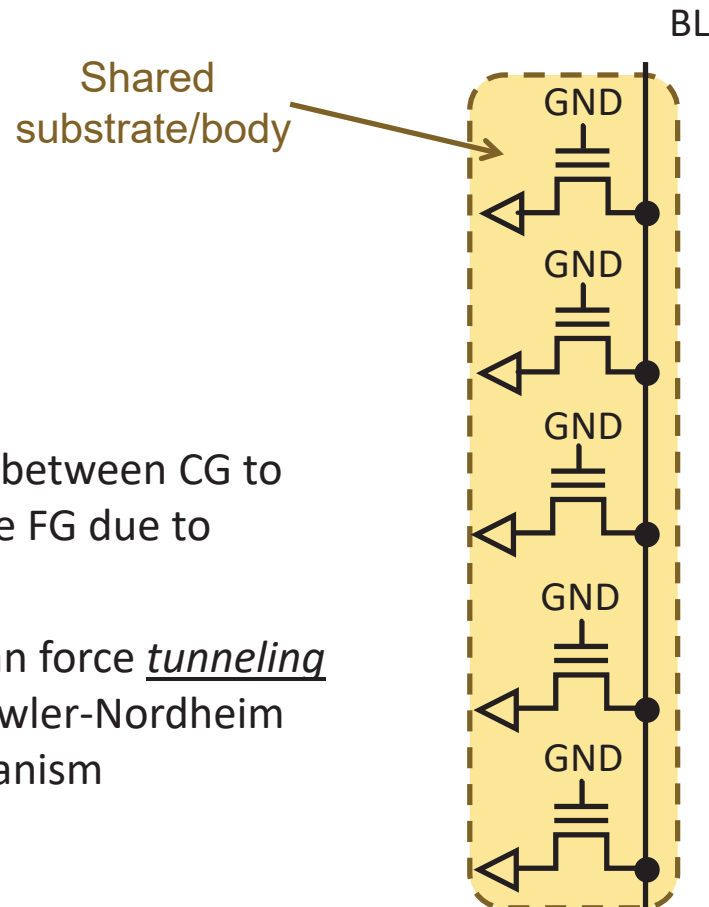Large electric field can force tunneling current to flow by Fowler-Nordheim (FN) tunneling mechanism




Main idea is the same as in NAND Flash: drive current between CG and substrate for a short period of time. Charges get trapped on the FG when current is abruptly turned off

PROGRAM operation:

- Set voltage of BL and substrate to GND
- Apply  $V_{PRG}$  to WL of selected bitcell

# Write Operations in NOR Flash

 

BL: Bit Line  
SL: Select Line  
WL: Word Line

High resistance path between CG to substrate through the FG due to insulating oxide


Large electric field can force tunneling current to flow by Fowler-Nordheim (FN) tunneling mechanism

Main idea is the same as in NAND Flash: drive current between CG and substrate for a short period of time. Charges get trapped on the FG when current is abruptly turned off

PROGRAM operation:

- Set voltage of BL and substrate to GND
- Apply  $V_{PRG}$  to WL of selected bitcell

# Write Operations in NOR Flash

 

BL: Bit Line

SL: Select Line

WL: Word Line

High resistance path between CG to substrate through the FG due to insulating oxide

Large electric field can force tunneling current to flow by Fowler-Nordheim (FN) tunneling mechanism

Main idea is the same as in NAND Flash: drive current between CG and substrate for a short period of time. Charges get trapped on the FG when current is abruptly turned off


PROGRAM operation:

- Set voltage of BL and substrate to GND
- Apply  $V_{PRG}$  to WL of selected bitcell

(block) ERASE operation:

- Set voltage of all WLs to GND
- Apply  $V_{ERS}$  to BL, substrate, and virtual GND

# Write Operations in NOR Flash

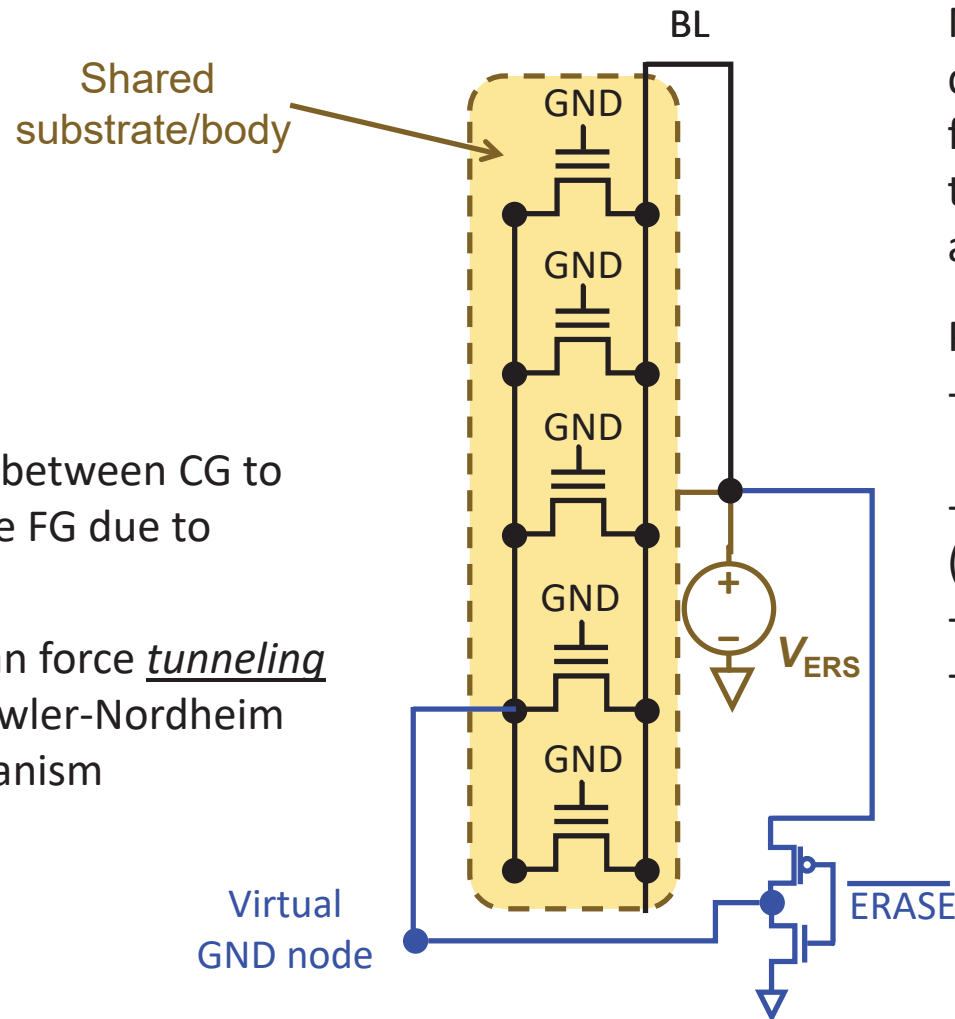

BL: Bit Line  
SL: Select Line  
WL: Word Line

High resistance path between CG to substrate through the FG due to insulating oxide

Large electric field can force tunneling current to flow by Fowler-Nordheim (FN) tunneling mechanism

Main idea is the same as in NAND Flash: drive current between CG and substrate for a short period of time. Charges get trapped on the FG when current is abruptly turned off

PROGRAM operation:

- Set voltage of BL and substrate to GND

- Apply  $V_{PRG}$  to WL of selected bitcell (block) ERASE operation:


- Set voltage of all WLs to GND
- Apply  $V_{ERS}$  to BL, substrate, and virtual GND

# Write Operations in NOR Flash

BL: Bit Line  
SL: Select Line  
WL: Word Line

High resistance path between CG to substrate through the FG due to insulating oxide

 Large electric field can force tunneling current to flow by Fowler-Nordheim (FN) tunneling mechanism



Main idea is the same as in NAND Flash: drive current between CG and substrate for a short period of time. Charges get trapped on the FG when current is abruptly turned off

PROGRAM operation:


- Set voltage of BL and substrate to GND
- Apply  $V_{PRG}$  to WL of selected bitcell

(block) ERASE operation:


- Set voltage of all WLs to GND
- Apply  $V_{ERS}$  to BL, substrate, and virtual GND
  - BL and virtual GND voltage cannot be GND or the pn-junctions with substrate will conduct leakage current

# Characteristics of Flash Memory

## NAND Flash

 

## NOR Flash

 

	NAND	NOR
<b>Speed</b>	X	O
<b>Density</b>	O	X
<b>Program</b>	Cell	
<b>Erase</b>	Block	

Memory management needed to:

- Map memory addresses to physical blocks of memory
  - Redundant blocks are needed
  - When erase operation is needed for a cell, entire block is marked as 'dirty' and copied to a 'clean' block
- Wear-leveling
  - Each cell can only support  $< \sim 10^6$  PROGRAM and ERASE ops.