


**National University of Singapore**  
**Electrical and Computer Engineering**

**CG2027 (Transistor-Level Digital Circuits)**  
**Assignment #4 Solution**

AY21/22 Semester 1  
 Issued: Aug. 31, 2021

Due: Sep. 05, 2021 (18:00)

 **Problem 1: Propagation delay of ripple-carry adder**



Derive the values of  $A_k$  and  $B_k$  ( $k=0 \dots N-1$ ) so that the worst case delay is obtained for the ripple-carry adder shown above.

→ Observing the figure, the worst case delay occurs when the carry is generated from the Least Significant Bit (LSB)  $C_{o,0}$ , then it ripples through all bit stages, from which finally  $C_{o,k}$  is generated.

→ If we assume  $C_{i,0}$  is 0, and initial value of  $S_{N-1}$  is 0,  $A_0$  and  $B_0$  must be 1. All the other stages must be in **propagate** mode. Hence, either  $A_i$  or  $B_i$  must be 1. Since the initial value of  $S_{N-1}$  is 0, we should also arrange a  $0 \rightarrow 1$  transition in SUM as well. This is achieved by setting both  $A_{N-1}$  and  $B_{N-1}$  to 0 (or 1), which yields a high sum bit given the incoming carry  $C_{o,k-1}$  of 1.

→ If we assume  $C_{i,0}$  is 1, then one of (but not both)  $A_0$  and  $B_0$  must be 1.

→ For example,  $\{A, B\} = \{00000001, 01111111\}$  is *one* of such combination. Note any  $\{A, B\}$  combination that satisfies aforementioned criteria yields the worst case delay.

**Problem 2: Ripple carry vs. Carry select adder**

- (a) Determine the worst-case delay of a 16-bit carry select adder. Assume  $t_{\text{setup}} = t_{\text{sum}} = 2$ , and  $t_{\text{carry}} = t_{\text{mux}} = 1$ . Compare this with the worst-case delay of a 16-bit ripple carry adder.

→ From the lecture, we note the delay of an N-bit linear carry-select adder with M-bits per stage is:

$$t_{\text{add}} = t_{\text{setup}} + M t_{\text{carry}} + \left(\frac{N}{M}\right) t_{\text{mux}} + t_{\text{sum}}, \text{ so } t_{\text{add}} = 2 + M + (16/M) + 2 = 4 + M + 16/M$$

We also note that the N-bit ripple carry adder is:

$$t_{add,ripple-carry} = (N - 1)t_{carry} + t_{sum}, \text{ so } t_{add,ripple-carry} = 17.$$

Comparing both, we can find that under given circumstances, if  $M \geq 2$ , the carry select adder has less propagation delay than that of the ripple-carry adder.

- (b) If each stage has 4 bits, what is minimum number of bits (N) do we need to have, in order for the carry-select adder to start showing less delay (when compared to a ripple-carry adder)? Assume  $t_{setup} = t_{sum} = 2$ , and  $t_{carry} = t_{mux} = 1$ .

➔ From the equations in (a), we let  $M=4$ .

$$T_{add,carry-select} = 2 + 4*1 + (N/4)*1 + 2 = (N/4) + 8$$

$$T_{add,ripple-carry} = (N-1)*1 + 2 = N + 1$$

We let  $T_{add,carry-select} \leq T_{add,ripple-carry}$ .  $(N/4) + 8 \leq N + 1$ . Therefore,  $N \geq 9.3333... \rightarrow$  If  $N \geq 10$ , then the carry-select adder has less delay. Therefore,  $N=10$ .

Note, in an actual adder implementation, in case N is not multiples of M (such as  $N=10$ ,  $M=4$  shown above), then the number of muxes in a carry-select adder should be rounded up from  $(N/M)$ . When we input  $N=10$  and  $M=4$ , we will need 3 muxes; in such case the delay of ripple carry and carry select adder delay to be 11. Therefore, more accurate answer will be  $N \geq 11$ .

We will consider both  $N=10$  and  $N=11$  as correct answers.