 


# ***CG2027 Transistor-Level Digital Circuits***

## ***Handout #2: CMOS Inverter***

**National University of Singapore  
Kelvin Fong**

# Design Abstraction Levels



# Lecture Overview


---

In this lecture, you will learn about

- Basic CMOS inverter
- Analyze switching and speed of the inverter
- Designing an inverter cell
 
# Basic Notations



- In CMOS technologies, both n-type (n-channel) and p-type (p-channel) Metal-Oxide-Semiconductor field-effect transistors (MOSFETs) are used.
- For MOSFETs, S denotes Source, D the Drain, G the Gate and B the body or substrate terminals. Small or capital letters are equivalent for voltages.



- n-type transistor : substrate is p-doped (acceptor type) and is connected to -ve supply  $V_{SS}$  (usually 0V or ground denoted as GND).
- For simplicity, as substrate bias is usually fixed, removal of substrate (body) contact leads to the compact notation on the right.
  
# Basic Notations


- p-type transistor : substrate is n-doped (donor type) and is connected to +ve supply (usually power supply voltage  $V_{DD}$ ).
- For simplicity, as substrate bias is usually fixed, removal of substrate (body) contact leads to the compact notation on the right.





Bubble denotes  
“active low”

# The CMOS Inverter: A First Glance

---

 


# CMOS Inverter

  

 
# Basic Notations

- The following circuit shows another way to represent 4 terminal MOS device (MOSFET).
- Basic simplest circuit block in CMOS technology is an inverter that uses both devices. The schematic of CMOS inverter is shown below.






# Basic n-channel MOS Device Description

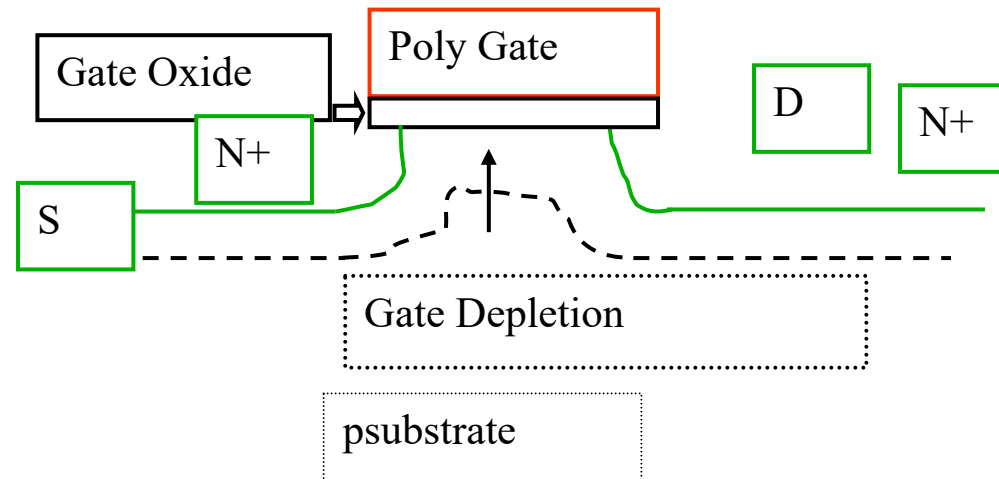


- Physical structure of MOSFET is very different as seen in earlier lectures and is schematically shown as above. The carriers are holes below the gate naturally and are positively charged.
- However, MOSFET conduction is done by electrons. Thus, the surface below the gate is inverted and electrons will be present when MOSFET is turned on. The MOSFET turns on when  $V_{gs}$  is above a predefined threshold voltage  $V_t$ .
- Source and Drain have a large number of electrons indicated with N+ symbol.
- If  $V_{gs}$  is negative, positively charged holes in the substrate will be attracted to Si-SiO<sub>2</sub> interface. Accumulation.

# Basic n-channel MOS Device Description

 

- As  $V_{GS}$  increases, the interface comes out of accumulation and holes are repelled and depleted below the gate oxide. The gate depletion (or space charge region) shown by dashed line under the gate becomes deeper with increasing  $V_{gs}$  as more holes will now be depleted.
- If  $V_{GS}$  increases further, eventually the device enters the regime of **strong inversion** where there is a large electron concentration (opposite to the substrate carriers holes) below the oxide. In effect strong electric field of the gate attracts electrons from the source into the channel. The gate depletion now stops deepening. The threshold voltage  $V_t$  of MOS device is defined as the  $V_{gs}$  that leads to strong inversion. After this  $V_{gs}$ , the device conducts with the help of the electrons in source, below the oxide and drain for positive  $V_{ds}$ .

# Basic n-channel MOS Device Description

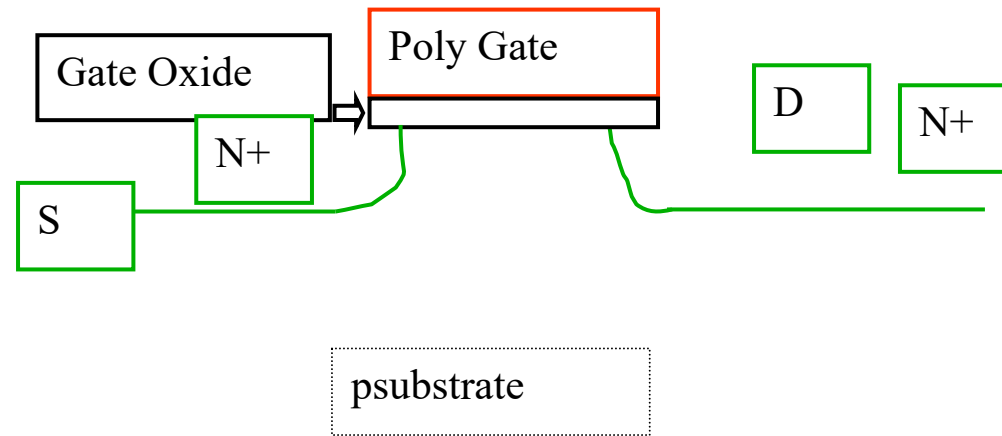


- Thin gate oxide always desirable for better gate control as lower thickness brings the gate closer to the conduction channel. As thin as 1.2 nm for technologies below 0.1 micron (13nm today).
- Polysilicon gate helped to achieve better process integration in the past. Metal gate and high-k gate oxide help in the current technologies.
- Large electron concentration source drain regions for low resistance.
- Low resistance metal connections for source, drain, body (same as substrate or well or tub - different notations).

# Basic n-channel MOS Device Description

- P-channel device has opposite relative voltages, has P+ (heavily p doped) source-drains, and n-type substrate. Both devices are used in CMOS technology which is our focus. P-channel device normally carries less current for similar dimension and voltages compared to n-channel due to lower mobility of holes.
- For designers, it is important to know how the drain current  $I_D$  changes when device dimensions,  $V_{GS}$  and  $V_{DS}$  change. Under simplified assumptions, analytic expressions for this current can be derived which we will use for design
- I-V plots and analytic expressions will now be discussed followed by inverter cell design and timing calculations with parasitic (unwanted capacitors and resistors which cannot be eliminated) estimation.
- Much later, we will introduce basic knowledge on what determines device limitations and how to logically develop a digital a circuit to implement it in Silicon.

# MOS Transistor Characteristics

 

- Simple Model: cut-off region :  $V_{gs} - V_t < 0$

$$I_{ds} = 0$$

( $V_t$  is the threshold voltage, also denoted as  $V_{TN}$  for n-channel MOSFET and  $V_{TP}$  for p-channel MOSFET. Normally,  $V_{TN} > 0$  and  $V_{TP} < 0$ ).

In the linear region where  $0 \leq V_{ds} \leq (V_{gs} - V_t)$ , Also called Triode region.

$$I_{ds} = \beta \left[ (V_{gs} - V_t) V_{ds} - \frac{V_{ds}^2}{2} \right]$$

# MOS Transistor Characteristics

In the saturation region where  $V_{ds} \geq (V_{gs} - V_t) > 0$ ,

$$I_{ds} = \frac{\beta}{2} (V_{gs} - V_t)^2$$

$$\text{where } \beta = \frac{\mu \epsilon}{t_{ox}} \left( \frac{W}{L} \right)$$

$\mu$  : effective surface mobility of charge carrier.

$\epsilon$  : permittivity of gate insulator.


$t_{ox}$  : thickness of gate insulator.

$W$  : channel width.

$L$  : channel length.
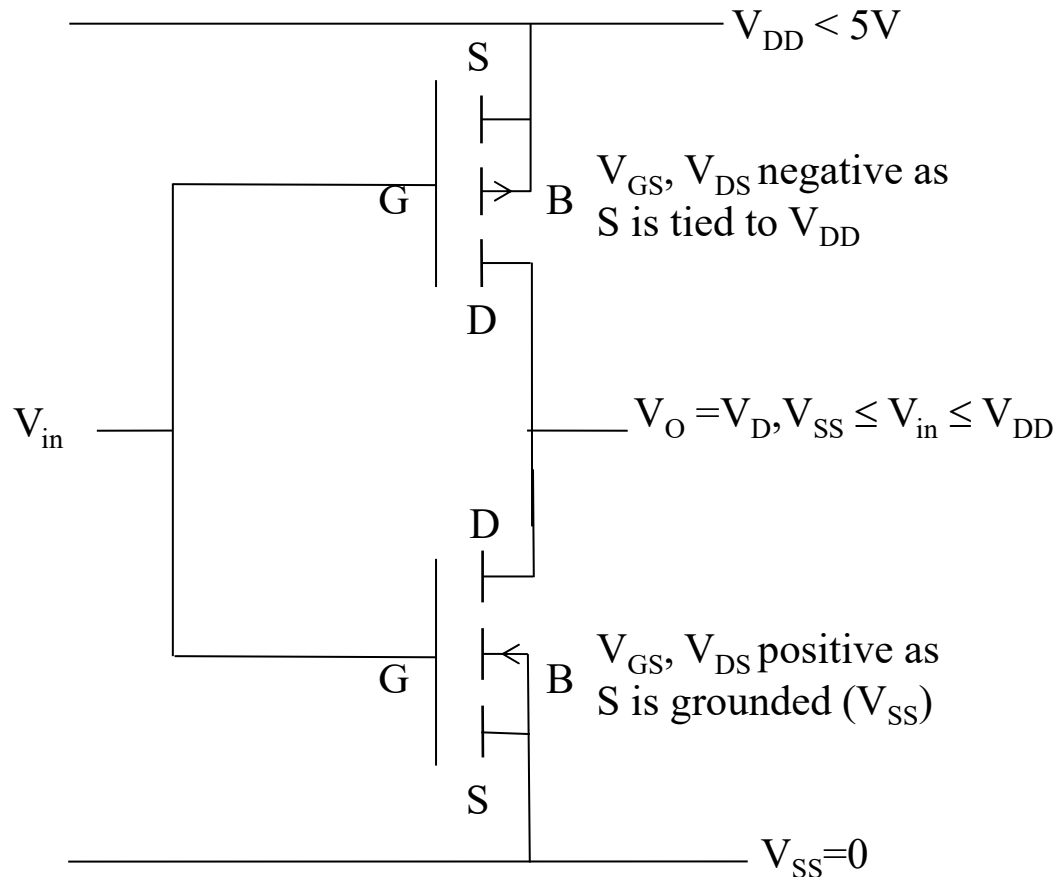
# Basic Operation of an Inverter

- The schematic of CMOS inverter is repeated below.



- If  $V_{in} = 0$ , then n-channel device is off.
- Hence there is no current through the n-channel device since it is like an OFF switch.
- For the p-channel device,  $V_{GS} = V_G - V_S = -V_{DD}$ . Hence, it is turned on.
- The only consistent voltage, where  $V_{GS} = -V_{DD}$  and p-channel device current is zero, is  $V_{DS} \text{ (p-channel)} = 0$  i.e.  $V_O = V_{DD}$ .
- Thus, if  $V_{in} = 0$ ,  $V_O = V_{DD}$ .

# Basic Operation of an Inverter


- On the other hand, if  $V_{in} = V_{DD}$ , then  $V_{GS} = 0$  for the p-channel device.
- Since  $V_{GS} \leq V_{TP}$  is a necessity for it to conduct, the device is off.
- Hence, there is no current through the n-channel device which is turned on by  $V_{in} = V_{DD} \geq V_{TN}$ .
- Again, for this to be consistent,  $V_{DS}$  (n-channel) = 0 or  $V_O = 0$ .
- Hence if  $V_{in} = V_{DD}$ ,  $V_O = 0$ .
- Thus it is clear that the circuit here performs a job of an inverter with  $V_{in} = 0$  or  $V_{in} = V_{DD}$ . When input switches from say 0 to  $V_{DD}$ , output switches from  $V_{DD}$  to 0.
- The devices are in different regions of operation during the switch. The switching of the inverter will be discussed later.



## Cross-section of CMOS Inverter

- Using simple isolation process, the inverter cross section including both NMOS and PMOS is as below.
- Two types of substrates.

### n-well process

 

Other processes :

p-well, twin-tub (more common),

SOI ( silicon on insulator )

p-substrate

*moderately doped*

*Oxide*

# Layout of Stand-alone CMOS Inverter

- Earlier, we drew a circuit of CMOS inverter and its cross section without worrying about how to make these devices and connect them on Silicon.
- Let us now discuss how many different layers will be needed on the layout at the minimum to achieve the cross section of inverter. Normally, many more layers are needed as there are additional steps and more than one metal layer.
- The starting substrate will normally have one type of doping. Here we use p-type substrate. Hence to make both p- and n-channel devices, we need to create an n-type regions using implant/diffusion in p-type substrate. This level is labeled as NWEL colored in brown.
- There should be a mask that defines gate regions using selective etching. This will normally be called as GATE or POLY mask named after polysilicon material normally used to form the gate.
- There should be a mask layer to form the N+ doped regions around the gate to make n-channel devices using implant/diffusion.

# Layout of Stand-alone CMOS Inverter

- There should be a mask layer to form the P+ doped regions around the gate to make p-channel devices using implant/diffusion.
- We need to connect these Source, Drain, Gate regions depending on the circuits to be implemented using [metal lines](#). These metal lines are isolated from each other by an insulator such as oxide. For this step, oxide is deposited over whole silicon substrate wafer and holes are made in it over S/D/G by etching to make actual connections by filling these holes with the metal. This is achieved using contact mask.
- We still need to connect these Source, Drain, Gate regions depending on the circuits to be implemented using metal lines. For this step, metal is deposited over whole silicon substrate wafer and the metal is etched from unwanted areas. This is achieved using metal mask.
- There can be several layers of contacts and metal mask pairs – up to 8 in advanced technologies. However, for simplicity, we will just confine to maximum 2 layers of metal.


# Layout of Stand-alone CMOS Inverter

- Also, note that many other considerations may add some process complexities or masks to the above basic set.
- The color convention is now given in the table for the minimum set. The convention for poly, N type active (S/D) area, contact and metal is universal. Others may vary a lot.

Layer	Color
NWEL	Brown
POLY (Gate)	Red
N+ (NSD-N type Source-Drain)	Green
P+ (PSD-P type Source-Drain)	Pink/Purple
CONT	Black
METAL	Blue

 
# Layout of Stand-alone CMOS Inverter

Layout diagram colour code in the process sequence order


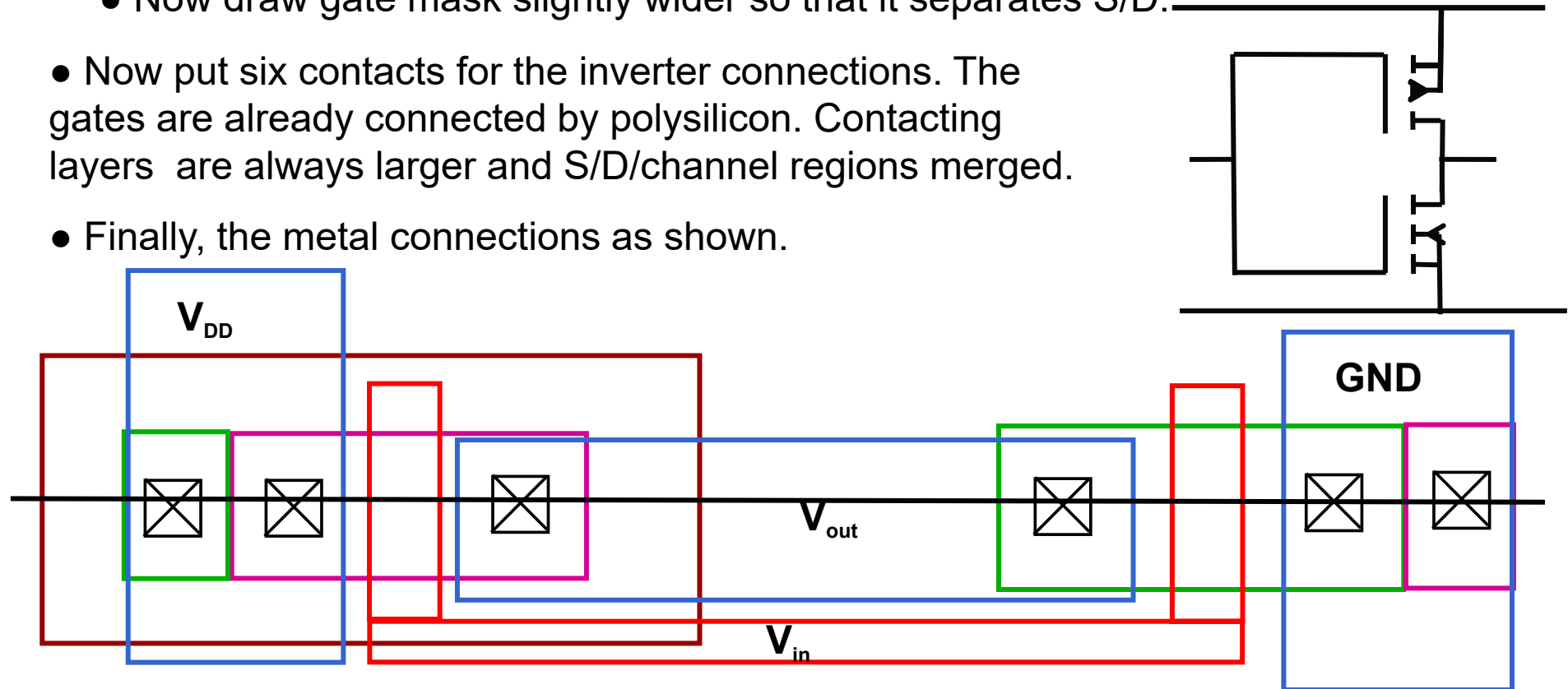
# Layout of Stand-alone CMOS Inverter

- Let us now evolve a primitive, stand alone, layout of the inverter.
- First form n-well which gives n-type substrate within p-type wafer. This has to accommodate all of p-type MOSFETs.
- Now form S/D regions for both devices. They should be wide enough to accommodate connections for the inverter and are continuous (slide-40).
- Now draw gate mask slightly wider so that it separates S/D.
- Now put six contacts for the inverter connections. The gates are already connected by polysilicon. Contacting layers are always larger and S/D/channel regions merged.
- Finally, the metal connections as shown.



# Switching Characteristics of the Inverter


- Now we study how regions of operations changes when inverter switches.

As  $V_{in}$  changes, these devices go through five different combinations of regions of operation. These combinations are indicated below.

1.  $0 \leq V_{in} \leq V_{TN}$  n-channel off, p-channel on
2.  $V_{TN} < V_{in} < V_{inv}$  p-channel linear, n-channel saturation
3.  $V_{in} = V_{inv}$  Both in saturation
4.  $V_{inv} < V_{in} < V_{DD} - V_{TP}$  n-channel linear, p-channel saturation
5.  $V_{DD} - V_{TP} \leq V_{in} \leq V_{DD}$  p-channel off, n-channel on


Where  $V_{inv}$  is called as switching voltage. The characteristics are derived based on the fact that both MOSFETs in the inverter here carry the same amount of current.
 
# Plot of Switching Characteristics of the Inverter






# CMOS Inverter VTC

 
 
# Switching Characteristics of the Inverter

- The current flowing through the inverter can be read from the plot and is shown below.




- One can notice that for a step  $V_{in}$ , the current only flows for a short time. If input is changing in a finite time, the current will flow through the inverter, which peaks at  $V_{inv}$ .
- This inverter will consume lower amount of power compared to circuits that continuously conduct such as bipolar or NMOS, as there is no current for some voltages.

- If there is no switching (Idle), there is no power consumption, in principle, a huge benefit for VLSI which made CMOS dominant.

- In reality, there is some power consumption due to sub-threshold currents, reverse biased diode currents and continuous running clocks.
 
# Switching Characteristics of the Inverter

- A simplified Voltage Response or voltage transfer characteristics (VTC) is as shown.



- Most change occurs near  $V_{inv}$  as the current here is the largest and aids in a fast transition. The slope at any point on the curve is the gain and is much larger than unity in magnitude at the blue switching voltage point.

# Switching Characteristics of the Inverter

## Switching voltage of the inverter.

- At switching voltage, the saturation current of n- and p- channel devices are equal.
- Assume that the threshold voltages of n- and p- transistors have the same magnitudes. Then

For n-transistor in saturation,  $I = \frac{\beta_n}{2}(V_{in} - V_t)^2$

For p-transistor in saturation,  $I = \frac{\beta_p}{2}(V_{DD} - V_{in} - |V_t|)^2$

For switching at  $V_{in} = \frac{V_{DD}}{2}$ ,  $I = \frac{\beta_n}{2}\left(\frac{V_{DD}}{2} - V_t\right)^2 = \frac{\beta_p}{2}\left(\frac{V_{DD}}{2} - |V_t|\right)^2$


$$i.e. \beta_n = \beta_p$$

# Switching Characteristics of the Inverter

$$\beta_n = \beta_p \Rightarrow \frac{\mu_n \varepsilon}{t_{ox}} \frac{W_n}{L_n} = \frac{\mu_p \varepsilon}{t_{ox}} \frac{W_p}{L_p} \Rightarrow \frac{W_p}{W_n} = \frac{\mu_n}{\mu_p}$$

as normally  $L_n = L_p$  in CMOS digital design.

 $\therefore \frac{W_p}{W_n} \approx 2$  based on electron and hole mobilities.




- The effect of sizes is best depicted in the figure.

Any observations?
 
# Switching Characteristics of the Inverter

- Noise margin in digital circuits is very important and should be as large as possible. We have studied it earlier. Here  $V_{OL} = 0$ ,  $V_{OH} = V_{DD}$ .
- It can be easily deduced from output response as the output is not likely to switch if magnitude of  $dV_o/dV_{in}$  is  $<1$  as the output voltage  $V_o$  changes slowly with the input voltage  $V_{in}$ .




- $V_{IL}$  = maximum LOW input voltage
- $V_{IH}$  = minimum HIGH input voltage
- Noise margin ( low ) =  $V_{IL}$
- Noise margin ( high ) =  $V_{DD} - V_{IH}$


# Switching Characteristics of the Inverter
 
## Loaded CMOS inverter

- The above conditions in switching studies are all ideal. Normally, CMOS inverter will have parasitic resistances and capacitances attached to the output node. Hence principle of operation of inverter alters a bit.
- The capacitor loaded CMOS inverter and its response is shown below.




 - We define:  $t_d$  : delay time,  $t_f$  : fall time and  $t_r$  : rise time as before


 
# Switching Characteristics of the Inverter



- If input was at low voltage, the output is high and the capacitor  $C_L$  holds the charge to maintain this high voltage.
- If input now switches instantaneously to high, the capacitor voltage does not change instantaneously as this requires infinite current. Instead, at the switching time, both the gate voltage and the drain voltage are high for the NMOS transistor which turns on.



- The NMOS device current will discharge the capacitor to zero after a delay time. This is why NMOS device is called as a pull down device.
- Once the output voltage reaches zero, NMOS transistor stops conducting as  $V_{DS} = 0$ . The output stays at zero volts after this delay and there is no current flowing through any part of the circuit.
- Exactly opposite cycle occurs when input becomes low and PMOS device charges the capacitor to raise output voltage to the power supply voltage. Similarly, PMOS device is called as a pull up device.




# CMOS Inverter: First-Order DC Analysis

  


$$\begin{aligned} V_{OL} &= 0 \\ V_{OH} &= V_{DD} \\ V_M &= f(R_n, R_p) \end{aligned}$$

**No Static Power Dissipation (ideally)**

# CMOS Inverter: Transient Response

 

(a) Low-to-high

 

(b) High-to-low

# POWER DISSIPATION

# Where Does Power Go in CMOS?

- **Dynamic Power Consumption**

Charging and Discharging Capacitors


- **Short Circuit Currents**

Short Circuit Path between Supply Rails during Switching

- **Leakage**

Leaking diodes and transistors

# Dynamic Power Dissipation

 

$$E_{VDD} = \int_0^{\infty} i_{VDD}(t) * V_{DD} dt$$

$$E_{C_L} = \int_0^{\infty} i_{VDD}(t) * v_{out} dt$$


$$\text{Energy/transition} = C_L * V_{dd}^2$$

$$\text{Power} = \text{Energy/transition} * f = C_L * V_{dd}^2 * f$$

$$q = CV$$
$$i = dq/dt = \text{CdV/dt}$$

- Not a function of transistor sizes if  $C_L$  dominated by connection metal!
- Need to reduce  $C_L$ ,  $V_{dd}$ , and  $f$  to reduce power.
 
# Modification for Circuits with Reduced Swing



$$E_{0 \rightarrow 1} = C_L \cdot V_{dd} \cdot (V_{dd} - V_t)$$

- Can exploit reduced swing to lower power (e.g., reduced bit-line swing in memory)

# Node Transition Activity and Power

- Consider switching a CMOS gate for  $N$  clock cycles

$$E_N = C_L \cdot V_{dd}^2 \cdot n(N)$$

$E_N$  : the energy consumed for  $N$  clock cycles

$n(N)$ : the number of 0→1 transition in  $N$  clock cycles

$$P_{avg} = \lim_{N \rightarrow \infty} \frac{E_N}{N} \cdot f_{clk} = \left( \lim_{N \rightarrow \infty} \frac{n(N)}{N} \right) \cdot C_L \cdot V_{dd}^2 \cdot f_{clk}$$


$$\alpha_{0 \rightarrow 1} = \lim_{N \rightarrow \infty} \frac{n(N)}{N}$$

$$P_{avg} = \alpha_{0 \rightarrow 1} \cdot C_L \cdot V_{dd}^2 \cdot f_{clk}$$

# CMOS Inverter Propagation Delay
 
## Approach 1 (Current Avg)

$$t_p = C_L \int_{v_1}^{v_2} \frac{dv}{i(v)} \quad \Rightarrow \quad t_p = \frac{C_L (v_2 - v_1)}{I_{av}}$$




$$t_{pHL} = \frac{C_L V_{swing}/2}{I_{av}}$$

$$\sim \frac{C_L}{\beta_n V_{DD}}$$


**Note)  $t_p$ : 50% of full swing**


 
# CMOS Inverter Propagation Delay Approach 2 (RC relaxation)


 
$$t_{pHL} = f(R_{on} \cdot C_L) \\ = 0.69 R_{on} C_L$$



**$\ln(2) = 0.69$  for  $0 \rightarrow 50\%$**   
 **$\ln(9) = 2.2$  for  $10\% \rightarrow 90\%$**

**Note)  $t_{pLH} = 0.69 R_{on,p} C_L$**


# **LOAD (CAPACITANCE / RESISTANCE)**

# Load Estimation

- **Load capacitance estimation**

- When a CMOS gate drives another CMOS gate, the driver "sees" a capacitive load. The load capacitance consists of

 
- (1) gate capacitance of the load from two MOSFETs on the right,
- (2) junction capacitance from common Drain of the driver inverter on the left,
- and
- (3) the parasitic routing capacitance from the metal line used for connection.



# Load Estimation

• Gate capacitances actually depend on terminal voltages. The simplest estimation in different regions is below. However many times a constant value is used.


• In summary

 

Parameter	Capacitance		
	Off	Linear	Saturation
$C_{gb}$	$\frac{\epsilon_{siO_2} A}{t_{ox}}$	0	0
$C_{gs}$	0	$\frac{\epsilon_{siO_2} A}{2t_{ox}}$	$\frac{2\epsilon_{siO_2} A}{3t_{ox}}$
$C_{gd}$	0	$\frac{\epsilon_{siO_2} A}{2t_{ox}}$	0
 
# Load Estimation

- **Source or drain junction capacitance estimation (2)**



- Peripheral capacitance is determined by the perimeter of Source or Drain whereas the area capacitance is determined by the area. Both area and perimeter are determined from the geometry of source or drain in the circuit layout which we have seen earlier.
- The total junction capacitance  $C_j$  is given by

$$C_j = area * C_{ja0} \left(1 - \frac{V_j}{\phi}\right)^{-ma} + perimeter * C_{jp0} \left(1 - \frac{V_j}{\phi}\right)^{-mp}$$

# Load Estimation

- **Source or drain junction capacitance estimation (2)**

- The total junction capacitance  $C_j$  is given by

$$C_j = area * C_{ja0} \left(1 - \frac{V_j}{\phi}\right)^{-ma} + perimeter * C_{jp0} \left(1 - \frac{V_j}{\phi}\right)^{-mp}$$

- where  $C_{ja0}$  and  $C_{jp0}$  zero voltage junction capacitance per unit area and perimeter tabulated below, respectively.

$V_j$  is the voltage across junction. (+ve for forward bias. -ve for reverse bias (MOS case)).


$\phi$  = built-in junction potential  $\approx 0.6 \sim 0.9$  V.

ma, mp (Grading coefficients) =  $0.3 \sim 0.5$


Parameter	n-diffusion	p-diffusion
$C_{ja0}$	$0.1 \text{ fF}/\mu\text{m}^2$	$0.1 \text{ fF}/\mu\text{m}^2$
$C_{jp0}$	$0.9 \text{ fF}/\mu\text{m}$	$0.8 \text{ fF}/\mu\text{m}$

# Load Estimation: The Wire

---

 


**Schematics**

 


**Physical**

# Interconnect Impact on Chip

 

**0.35um 5M layers**

 


**14 nm (Intel's Broadwell / i7 6800k)**

e.g. TSMC's 28nm → 10 layers of Metal




# Capacitance of Wire Interconnect

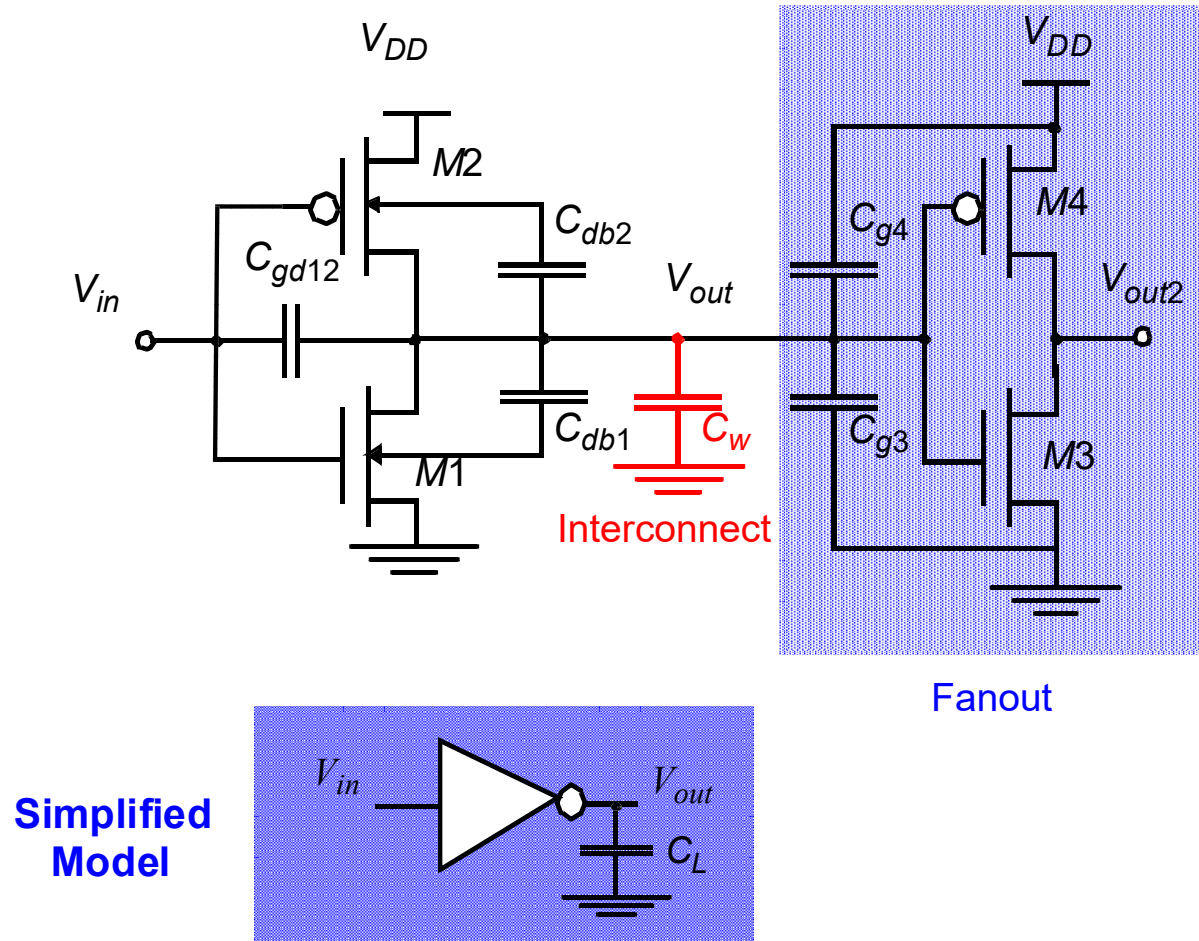

# Capacitance: The Parallel Plate Model

---

 

To calculate the parallel plate wire capacitance ( $C_{pp}$ ) for this segment (length  $L$ , width  $w$ )

$$C_{pp} = \frac{\epsilon_{di}}{t_{di}} WL$$


# Permittivity

---

Material	$\epsilon_r$
Free space	1
Aerogels	$\sim 1.5$
Polyimides (organic)	3-4
Silicon dioxide	3.9
Glass-epoxy (PC board)	5
Silicon Nitride ( $\text{Si}_3\text{N}_4$ )	7.5
Alumina (package)	9.5
Silicon	11.7

# Fringing Capacitance

---

 


Wire capacitance per unit length:

$$c_{wire} = c_{pp} + c_{fringe} = \frac{w\epsilon_{di}}{t_{di}} + \frac{2\pi\epsilon_{di}}{\log(t_{di}/H)}$$

To calculate the total wire capacitance, you can multiply  $c_{wire}$  by the length  $L$ .

# Fringing vs. Parallel Plate

 

(from [Bakoglu89])


# Wiring Capacitances

---

CAPACITANCE PARAMETERS	N+	P+	POLY	M1	M2	M3	M4	M5	M6	D_N_W	N_W	UNITS
Area (substrate)	963	1159	110	38	19	13	8	8	3		125	aF/um^2
Area (N+active)			8556	51	21	14	11	9	8			aF/um^2
Area (P+active)			8309									aF/um^2
Area (poly)				58	17	10	7	5	4			aF/um^2
Area (metal1)					41	15	10	7	5			aF/um^2
Area (metal2)						36	14	9	7			aF/um^2
Area (metal3)							39	15	9			aF/um^2
Area (metal4)								36	14			aF/um^2
Area (metal5)									37			aF/um^2
Area (r well)	987											aF/um^2
Area (no well)	143											aF/um^2
Fringe (substrate)	248	203		13	61	55	43	24				aF/um
Fringe (poly)				64	38	29	24	20	17			aF/um
Fringe (metal1)					61	34		23	19			aF/um
Fringe (metal2)						53	36	26	22			aF/um
Fringe (metal3)							54	34	28			aF/um
Fringe (metal4)								57	35			aF/um
Fringe (metal5)									53			aF/um
Overlap (P+active)			636									aF/um

# Example

---

 


**Area Capacitance**

**Fringe Capacitance**

# Wire Resistance

---

 



# Sheet Resistance


Material	Sheet Resistance ( $\Omega/\square$ )
n- or p-well diffusion	1000 – 1500
$n^+$ , $p^+$ diffusion	50 – 150
$n^+$ , $p^+$ diffusion with silicide	3 – 5
$n^+$ , $p^+$ polysilicon	150 – 200
$n^+$ , $p^+$ polysilicon with silicide	4 – 5
Aluminum	0.05 – 0.1

PROCESS PARAMETERS	N+	P+	POLY	N+BLK	PLY+BLK	M1	M2	UNITS
Sheet Resistance	6.6	7.6	7.7	60.1	312.5	0.08	0.08	ohms/sq
Contact Resistance	10.4	10.9	9.7				4.36	ohms
Gate Oxide Thickness	40							angstrom
PROCESS PARAMETERS	M3	POLY_HRI		M4	M5	M6	N_W	UNITS
Sheet Resistance	0.08	1304.6		0.07	0.07	0.04	913	ohms/sq
Contact Resistance	9.08			13.85	19.37	22.28		ohms

o

# Example

---

 

**Wire Resistance (long side)**

# Interconnect Resistance

---

Material	$\rho$ ( $\Omega\text{-m}$ )
Silver (Ag)	$1.6 \times 10^{-8}$
Copper (Cu)	$1.7 \times 10^{-8}$
Gold (Au)	$2.2 \times 10^{-8}$
Aluminum (Al)	$2.7 \times 10^{-8}$
Tungsten (W)	$5.5 \times 10^{-8}$

# Dealing with Resistance

---

- **Selective Technology Scaling**
- **Use Better Interconnect Materials**
  - reduce average wire-length
  - e.g. copper, silicides
- **More Interconnect Layers**
  - reduce average wire-length


# IR Drop

---

- Power ring design
  - Metal width
  - Choosing a metal layer

# CMOS INVERTER LAYOUT

# Inverter Layout: Standard Cells

 

Cell height 12 metal tracks

Metal track is approx.  $3\lambda + 3\lambda$



Pitch =  
repetitive distance between objects

Cell height is “12 pitch”


The design rules specify minimum dimensions and spacing. They are technology independent using a parameter  $\lambda$  which shrinks as technology scales.

# Standard Cells

With minimal  
diffusion  
routing

  


With silicided  
diffusion

 




# Standard Cells

 



2-input NAND gate

 

# Two Inverters


Share power and ground

Abut cells

  
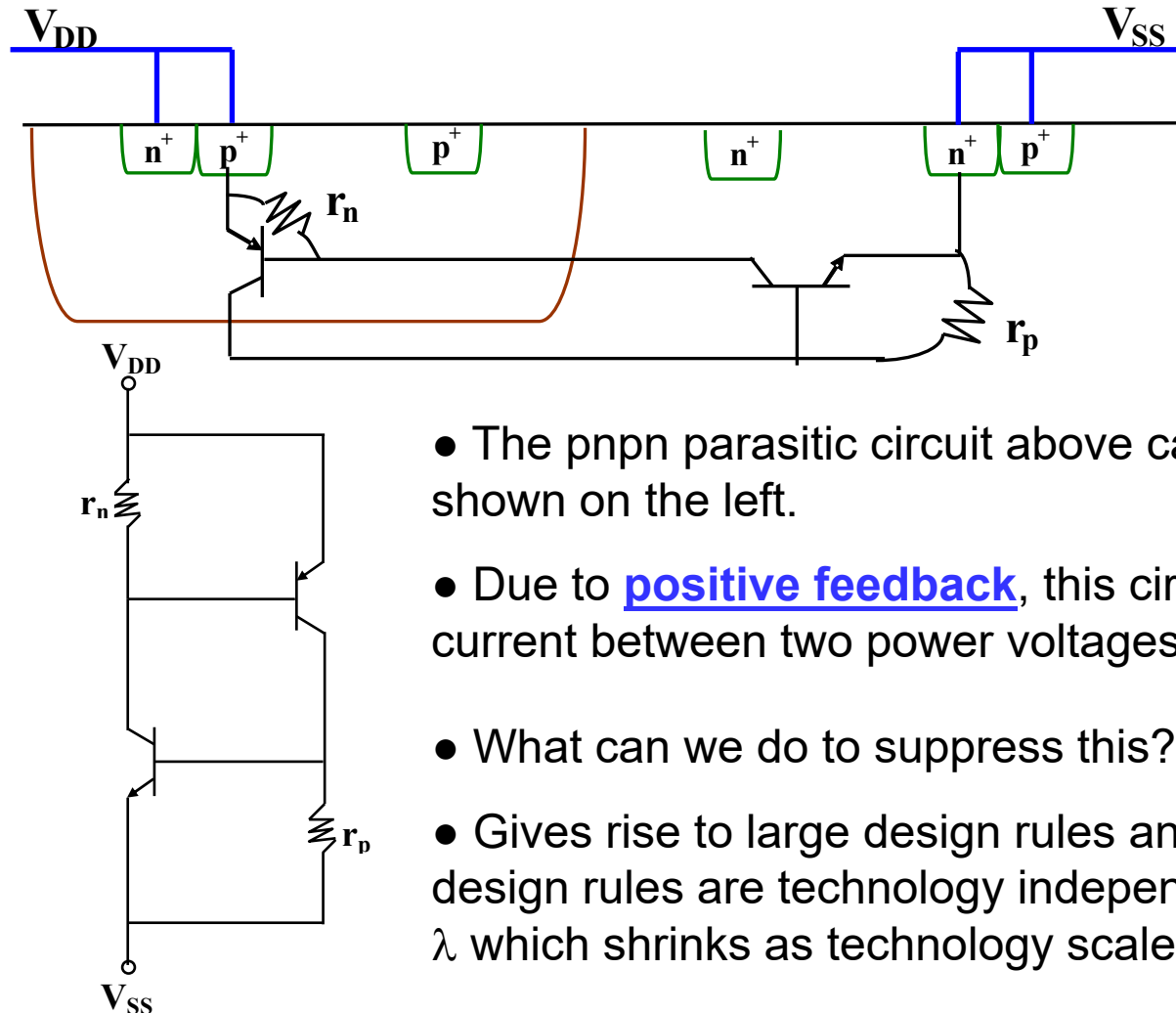
# CMOS Latch-up

- It is clear that we have got many parasitic devices along with the MOSFET in the cross-section. Here is one such parasitic p-n-p-n device which is responsible for latch-up reliability issue in CMOS. It has one npn and one pnp bipolar transistor and 2 resistors as shown.



- The pnpn parasitic circuit above can be re-arranged as shown on the left.
- Due to positive feedback, this circuit can conduct large current between two power voltages and gate is immaterial.
- What can we do to suppress this?
- Gives rise to large design rules and extra features. The design rules are technology independent using a parameter  $\lambda$  which shrinks as technology scales.