

National University of Singapore
Electrical and Computer Engineering

CG2027 (Transistor-Level Digital Circuits)
Assignment #3

AY21/22 Semester 1
 Issued: Aug. 24, 2021

Due: Aug. 29, 2021 (18:00)

Problem 1: CMOS Logic

Consider the following CMOS logic circuits:

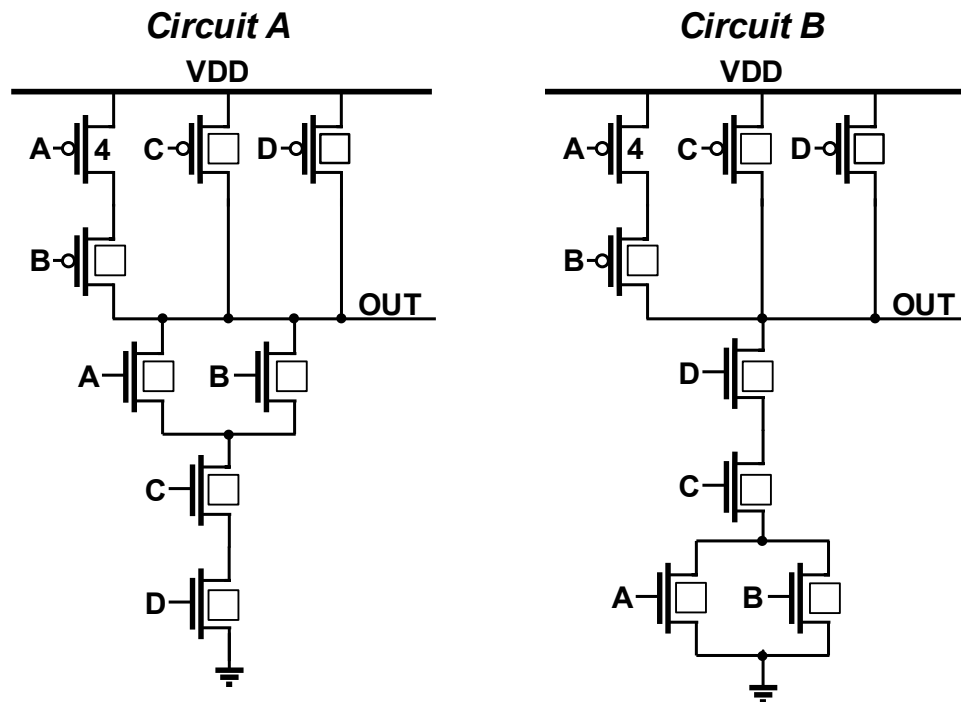


Figure 1: Two static CMOS gates.

- Provide the Boolean expression for the circuits in **Figure 1** and show whether they implement the same logic function.
- What is the appropriate transistor sizing for the logic circuit to have similar to 1X inverter delay? Fill in the empty boxes. Assume PMOS A has width of 4 (as shown above), and INV1X has $W_{PMOS}:W_{NMOS}$ of 2:1.
- Assume the transistors have been sized to give a worst case output resistance of 12kohm in both pull-up and pull-down networks for the worst-case input patterns. What input patterns (A-D) give the lowest output resistance when the output is low? What is the value of that resistance?
- What input patterns (A-D) give the lowest output resistance when the output is high? What is the value of that resistance?
- Neglecting parasitics and assuming a load capacitance of 100fF, calculate the best case t_{pLH} and t_{pHL} .

Problem 2: Pass Transistor Logic and Level Restoration

Consider the circuits of **Figure 2**. Assume the inverter of M1 and M2 switches ideally at $V_{DD}/2$, neglect body effect, channel length modulation and all parasitic capacitances throughout this problem. Use the parameters in the Table for NMOS and PMOS.

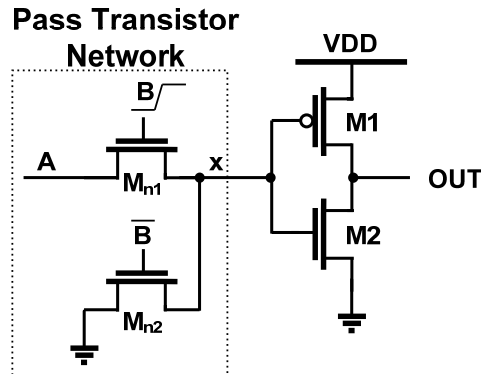


Figure 2: Level restoring circuit.

- What is the logic function performed by this circuit?
- Explain why this circuit has non-zero static power dissipation?
- Using only just 1 transistor, design a fix so that there will not be any static power dissipation. Explain how you chose the size of the transistor.
- Replace the pass-transistor network in **Figure 2** with a pass transistor network that computes the following function: $x=ABC$ at the node x. Assume you have the true and complementary versions of the three inputs A, B and C.