


**National University of Singapore**  
**Electrical and Computer Engineering**  
**CG2027 (Transistor-Level Digital Circuits)**  
**Assignment #1 Solution**

AY21/22 Semester 1  
 Issued: Aug. 10, 2021

Due: Aug. 15, 2021 (18:00)

 
**Problem 1: Delay Calculation**

The objective of this problem is to figure out correct delay / risetime / falltime of a CMOS inverter, based on the information given from the waveform.



- What is the rise time ( $t_r$ ), fall time ( $t_f$ ) of the output waveform  $V_{out}$ ?  
 $\rightarrow t_r = 383.86 - 359.95 = 23.92$  (ps),  $t_f = 132.36 - 113.35 = 19.01$  (ps)
- What is the high-to-low propagation delay ( $t_{pHL}$ ) of the logic?  $\rightarrow t_{pHL} = 120.88 - 108.62 = 12.26$  (ps)
- What is the low-to-high propagation delay ( $t_{pLH}$ ) of the logic?  $\rightarrow t_{pLH} = 368.35 - 355.05 = 13.30$  (ps)
- If the given waveform is the half of the clock cycle with 50% duty, what is the clock frequency?  
 $\rightarrow$  You can choose any half-clock cycle points. E.g.,  $350.43 - 101.80 = 248.63$  ps (half cycle),  $2 \times 248.63$  ps  $\approx 0.5$  ns (1 cycle). Therefore, the clock freq is approx. **2GHz** (note:  $\pm 5\%$  difference is allowed)

## Problem 2: Noise Margin

 

- a) For the inverter chain given above, calculate the noise margin high ( $NM_H$ ) and noise margin low ( $NM_L$ ).

$$\rightarrow NM_H = |V_{OH1} - V_{IH2}| = |0.85 - 0.75| = 0.10 \text{ (V)}$$

$$\rightarrow NM_L = |V_{OL1} - V_{IL2}| = |0.10 - 0.25| = 0.15 \text{ (V)}$$

- b) What happens if input high and input low of the Buf2 become the same? Explain.

$\rightarrow$  Noise margin high and noise margin low will be maximized.