

National University of Singapore
Electrical and Computer Engineering
CG2027 (Transistor-Level Digital Circuits)
Tutorial #3 Solution

AY21/22 Semester 1
Assigned: Aug. 24, 2021

Due: Aug. 29, 2021 (18:00)

Problem 1: CMOS Logic

Consider the following CMOS logic circuits:

 


Figure 1: Two static CMOS gates.

- Provide the Boolean expression for the circuits in **Figure 1** and show whether they implement the same logic function → Yes, same function. $\overline{OUT} = (A + B) \cdot C \cdot D$
- What is the appropriate transistor sizing for the logic circuit to have similar to 1X inverter delay? Fill in the empty boxes. Assume PMOS A has width of 4 (as shown above), and INV1X has $W_{PMOS}:W_{NMOS}$ of 2:1.
→ See the boxes above.
- Assume the transistors have been sized to give a worst case output resistance of 12kohm in both pull-up and pull-down networks for the worst-case input patterns. What input patterns (A-D) give the lowest output resistance when the output is low? What is the value of that resistance?
→ When output is low, the output resistance R_{OUT} is the lowest when ALL inputs are high, $\{A,B,C,D\}=\{1,1,1,1\}$.

→ $R_{OUT} = R_N + R_N + (R_N // R_N) = 12/3k + 12/3k + (12/3)/2k = 4k + 4k + 2k = 10k\Omega$.

- d) What input patterns (A-D) give the lowest output resistance when the output is high? What is the value of that resistance?

→ When output is high, the output resistance R_{OUT} is the lowest when ALL inputs are low, $\{A,B,C,D\} = \{0,0,0,0\}$.

→ $R_{OUT} = R_P // R_P // (1/2R_P + 1/2R_P) = 12k // 12k // 12k = 4k\Omega$.

- e) Neglecting parasitics and assuming a load capacitance of 100fF, calculate the best case t_{pLH} and t_{pHL} .

→ Refer to the Lecture 2 slide 34.

→ $t_{pLH,best} = 0.69 \cdot R_{PUN} \cdot C_L = 0.69 \cdot 4k \cdot 100f = 276 \text{ (ps)}$

→ $t_{pHL,best} = 0.69 \cdot R_{PDN} \cdot C_L = 0.69 \cdot 10k \cdot 100f = 690 \text{ (ps)}$

Problem 2: Pass Transistor Logic and Level Restoration

Consider the circuits of **Figure 2**. Assume the inverter of M1 and M2 switches ideally at $V_{DD}/2$, neglect body effect, channel length modulation and all parasitic capacitances throughout this problem. Use the parameters in the Table for NMOS and PMOS.


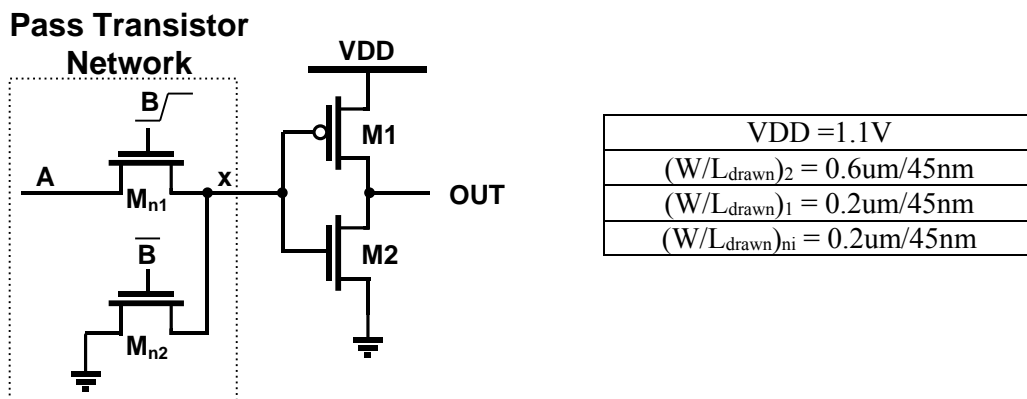


Figure 2: Level restoring circuit.

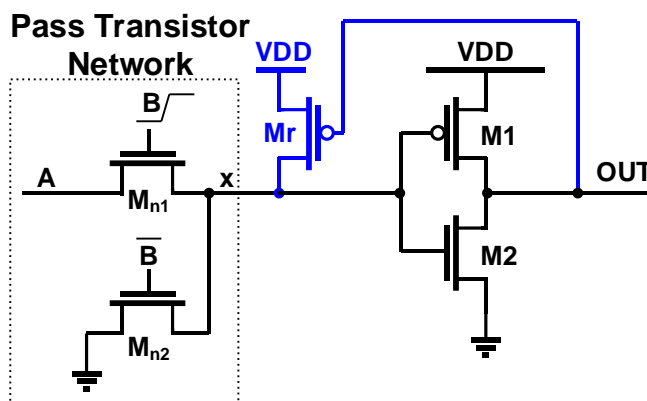- a) What is the logic function performed by this circuit?
 → **NAND**: Pass Transistor Network performs AND, then followed by an inverter (by M1 and M2).
- b) Explain why this circuit has non-zero static power dissipation?
 → When $A=B=1$, the pass transistor M_{n1} will pass only up to $V_{DD}-V_{th,nmos}$ to the node X. This causes M1 to not completely turn off, and hence both M1 and M2 will be marginally on; static power will be dissipated.
- c) Using only just 1 transistor, design a fix so that there will not be any static power dissipation. Explain how you chose the size of the transistor (use the parameters given above and show calculations).
 → We can add M_r as shown below.



- M_r should be sized small enough so that M_{n2} can pull the node x down to GND when B is 0. M_r conducts while switching which causes this problem to occur. As M_{n2} is $0.6\mu m/45nm$, M_r could be $0.1\mu m/45nm$ or even lower up to $45nm/45nm$ if allowed under design rules.
- d) Replace the pass-transistor network in **Figure 2** with a pass transistor network that computes the following function: $x=ABC$ at the node x . Assume you have the true and complementary versions of the three inputs A , B and C .
 → Note below answer is an example. B, C high gives output A and is 1 if $A=1$. If B or C is low, one of M_{n2} or M_{n3} or both will pull output low. Other pass transistor logic that makes $x=ABC$ out of $A, B, C, /A, /B, /C$ will be also correct.

